

# GE 104 : Introduction to electrical engineering

Dr. Sekhar

Power electronics lab






IIT Ropar

# 1. Energy and Power

$$v = \frac{dw}{dq} \quad v \text{ is voltage ; potential difference between two charge particle}$$



$$\text{Power } p = \frac{dw}{dt} = \left( \frac{dw}{dq} \right) \left( \frac{dq}{dt} \right) = vi$$

## 2. Sources and loads

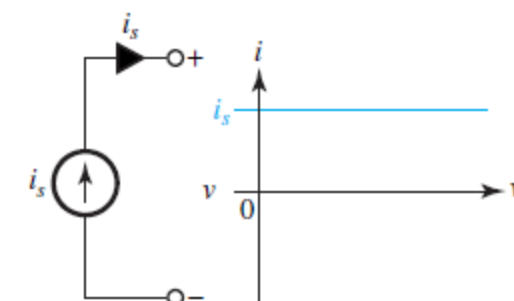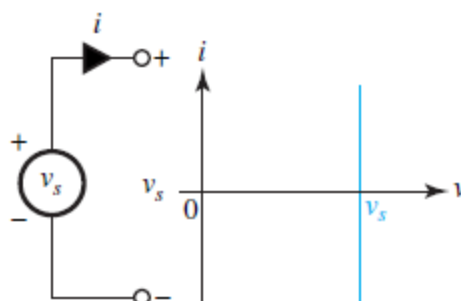
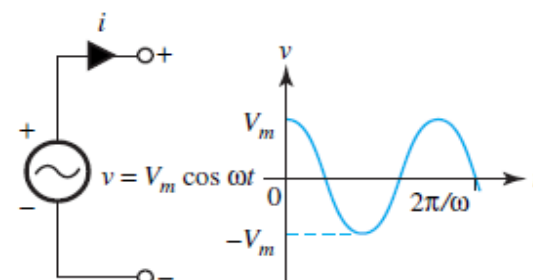
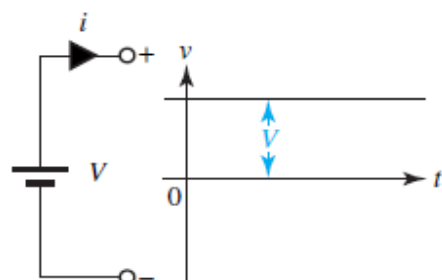
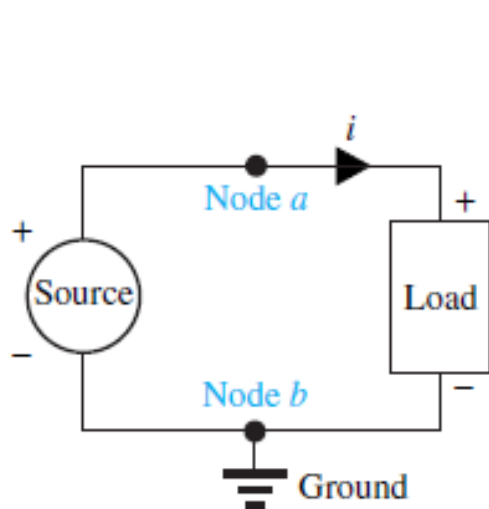


DC voltage ; AC voltage ; Ideal voltage and current source

# 3. Sources

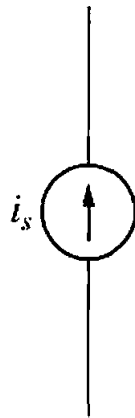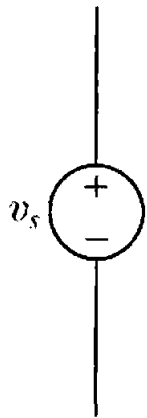


Idea Voltage and current source

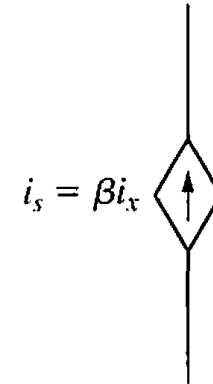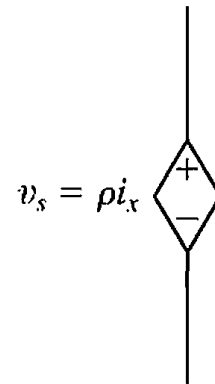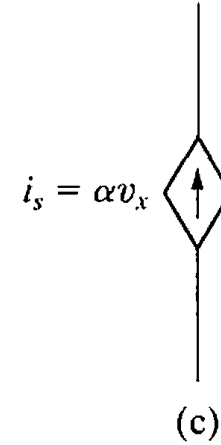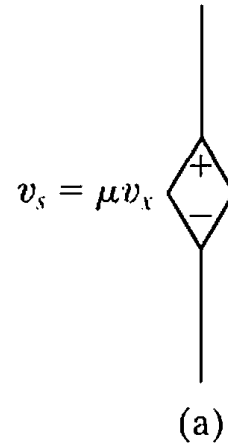

Dependant sources- (a) Voltage controlled voltage  
(b) Voltage controlled current (c) current controlled  
Voltage (d) current controlled current

## 4. Lumped Circuit Elements

- Resistance
- Inductance
- Capacitance

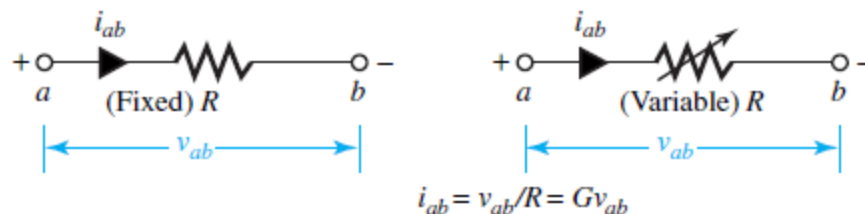

$$i = v/R = Gv, \text{ or } v = iR$$


$$R = \frac{\rho l}{A} = \frac{l}{\sigma A}$$

**Temperature dependency  
on resistivity**

$$\rho_{T2} = \rho_{T1} \left( \frac{T_2 + T}{T_1 + T} \right)$$

Type	Material	$\rho (\Omega \cdot \text{m})$
Conductors (at 20°C)	Silver	$16 \times 10^{-9}$
	Copper	$17 \times 10^{-9}$
	Gold	$24 \times 10^{-9}$
	Aluminum	$28 \times 10^{-9}$
	Tungsten	$55 \times 10^{-9}$
	Brass	$67 \times 10^{-9}$
	Sodium	$0.04 \times 10^{-6}$
	Stainless steel	$0.91 \times 10^{-6}$
	Iron	$0.1 \times 10^{-6}$
	Nichrome	$1 \times 10^{-6}$
	Carbon	$35 \times 10^{-6}$
	Seawater	0.25
Semiconductors (at 27°C or 300 K)	Germanium	0.46
	Silicon	$2.3 \times 10^3$
Insulators	Rubber	$1 \times 10^{12}$
	Polystyrene	$1 \times 10^{15}$



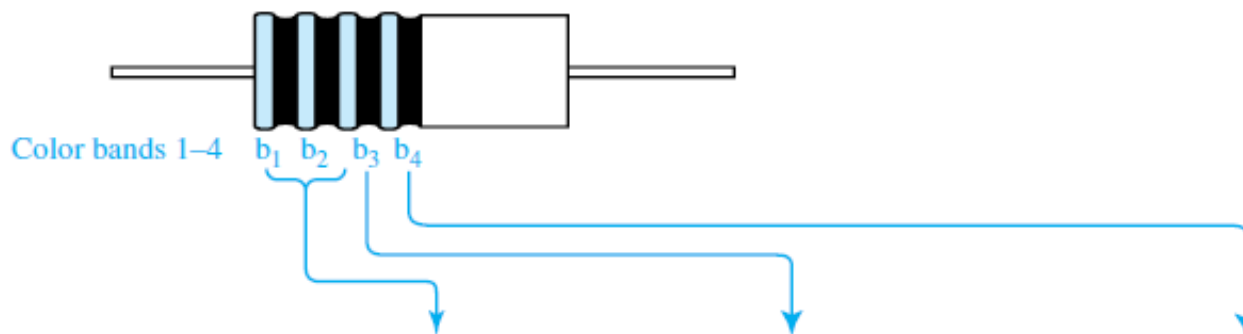
# 5. Lumped Circuit Elements (Resistance)



Color of Band	Digit of Band	Multiplier	% Tolerance in Actual Value
Black	0	$10^0$	—
Brown	1	$10^1$	—
Red	2	$10^2$	—
Orange	3	$10^3$	—
Yellow	4	$10^4$	—
Green	5	$10^5$	—
Blue	6	$10^6$	—
Violet	7	$10^7$	—
Grey	8	$10^8$	—
White	9	—	—
Gold	—	$10^{-1}$	$\pm 5\%$
Silver	—	$10^{-2}$	$\pm 10\%$
Black or no color	—	—	$\pm 20\%$


$$\text{Resistance value} = (10b_1 + b_2) \times 10^{b_3} \Omega.$$

# 5. Resistance (Parallel & series )

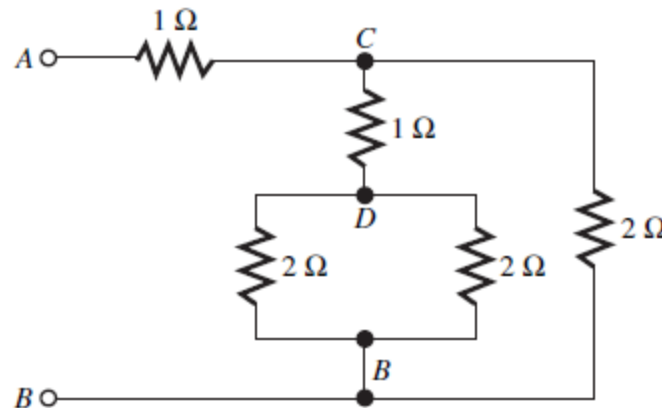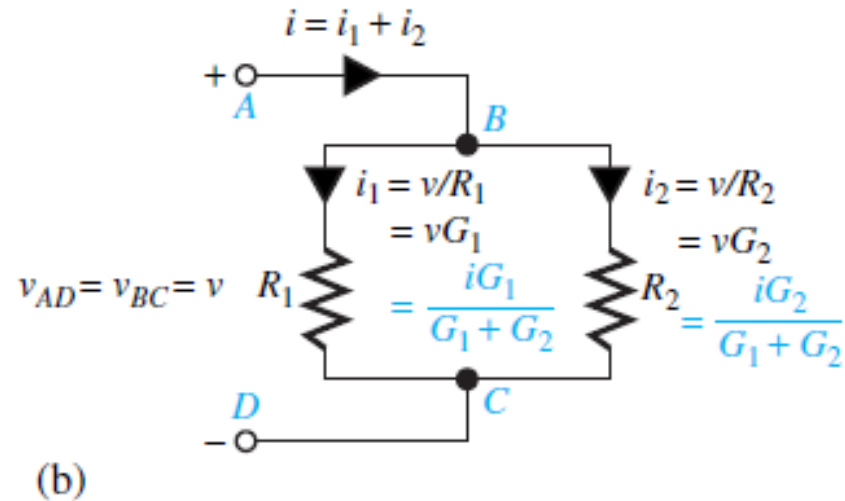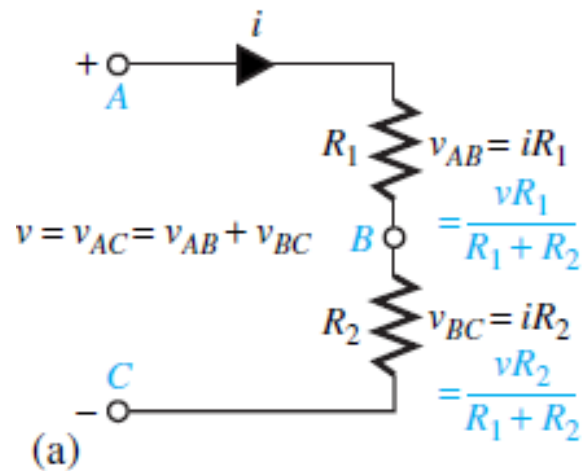

## 6. Kirchhoff's Laws


- kirchhoff's Current Law (KCL)*

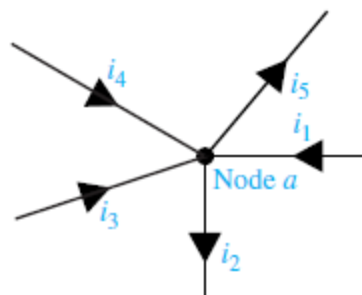

$$i_1 - i_2 + i_3 + i_4 - i_5 = 0 \quad \text{or} \quad -i_1 + i_2 - i_3 - i_4 + i_5 = 0$$

$$\text{or} \quad i_1 + i_3 + i_4 = i_2 + i_5$$


- kirchhoff's Voltage Law (KVL)*

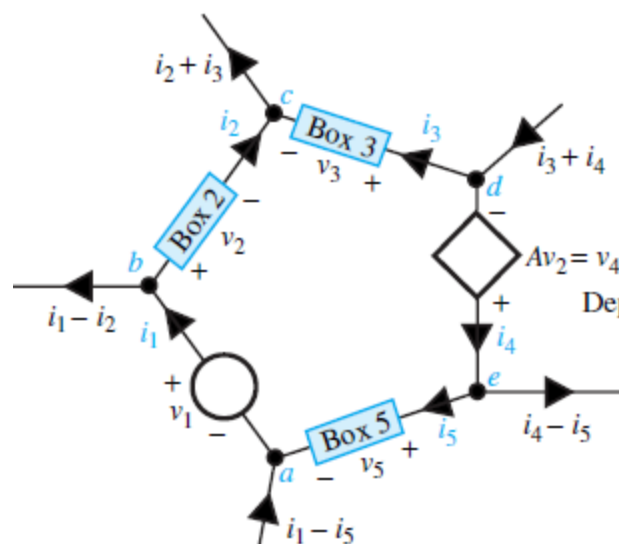

$$-v_1 + v_2 - v_3 - v_4 + v_5 = 0 \quad \text{or} \quad v_1 - v_2 + v_3 + v_4 - v_5 = 0$$

$$\text{or} \quad v_1 + v_3 + v_4 = v_2 + v_5$$

## 6. Example

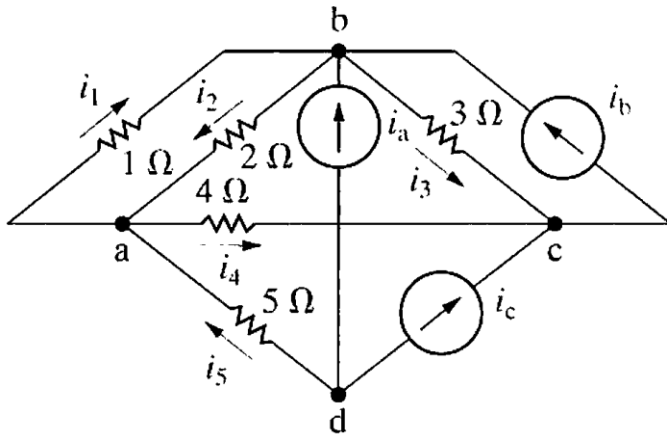


node a  $i_1 + i_4 - i_2 - i_5 = 0,$

node b  $i_2 + i_3 - i_1 - i_b - i_a = 0,$

node c  $i_b - i_3 - i_4 - i_c = 0,$

node d  $i_3 + i_a + i_c = 0.$

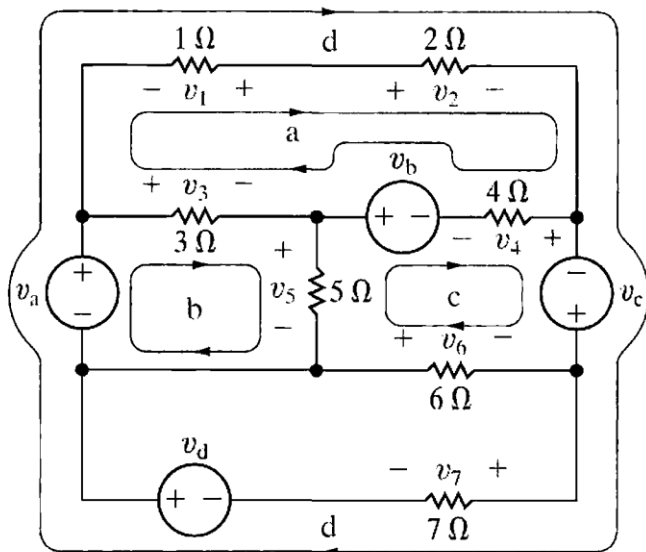

path a  $-v_1 + v_2 + v_4 - v_b - v_3 = 0,$


path b  $-v_a + v_3 + v_5 = 0,$

path c  $v_b - v_4 - v_c - v_6 - v_5 = 0,$

path d  $-v_a - v_1 + v_2 - v_c + v_7 - v_6 = 0.$




## 6. Example

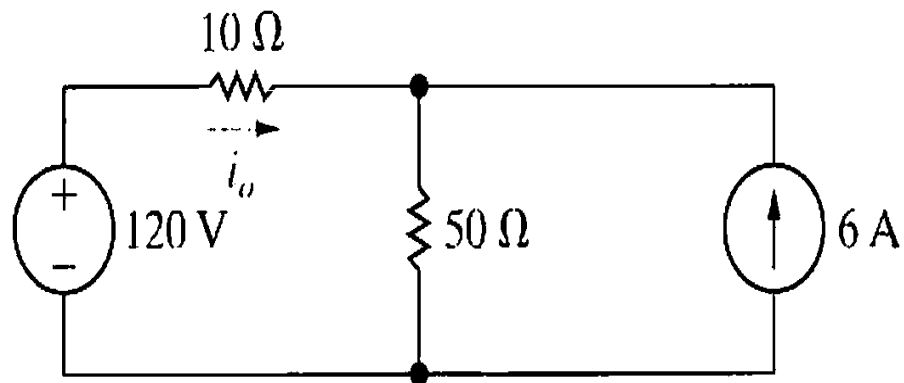


$$i_1 - i_o - 6 = 0.$$

$$-120 + 10i_o + 50i_1 = 0.$$
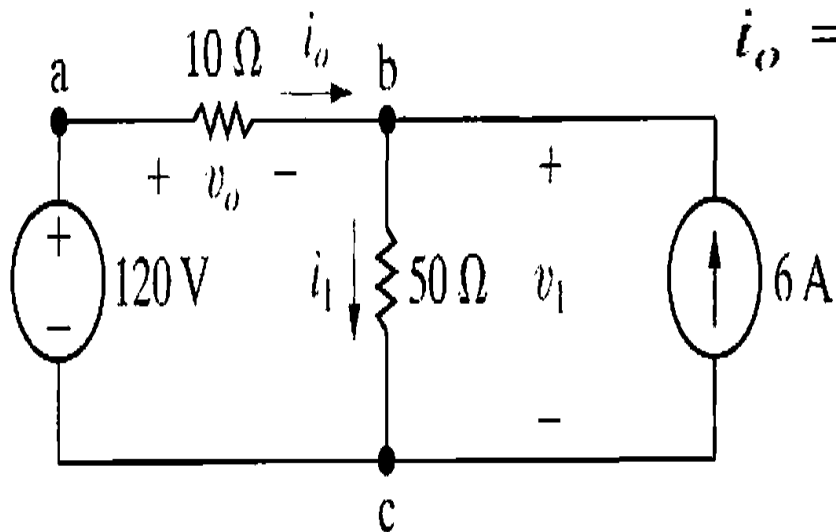
$$i_o = -3 \text{ A} \quad \text{and} \quad i_1 = 3 \text{ A}.$$



## 6. Example –Dependant source

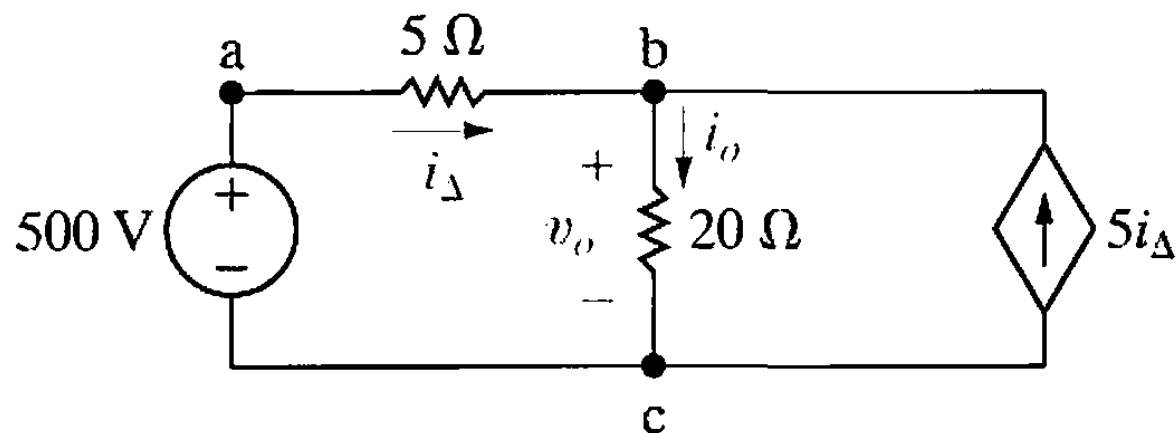


$$500 = 5i_{\Delta} + 20i_o.$$

$$i_o = i_{\Delta} + 5i_{\Delta} = 6i_{\Delta}.$$


$$i_{\Delta} = 4\text{ A},$$

$$i_o = 24\text{ A}.$$

# 7. Nodal Analysis

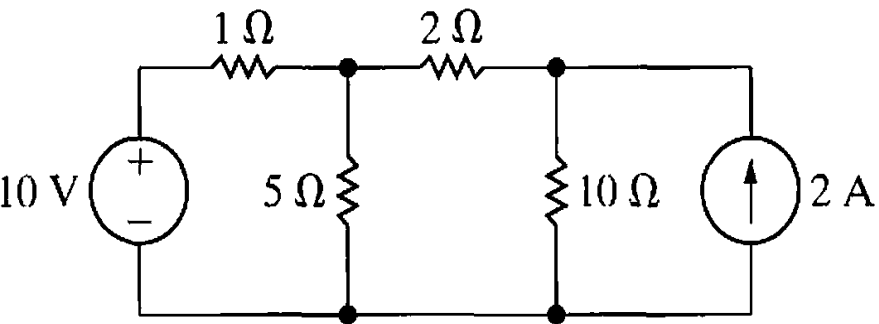
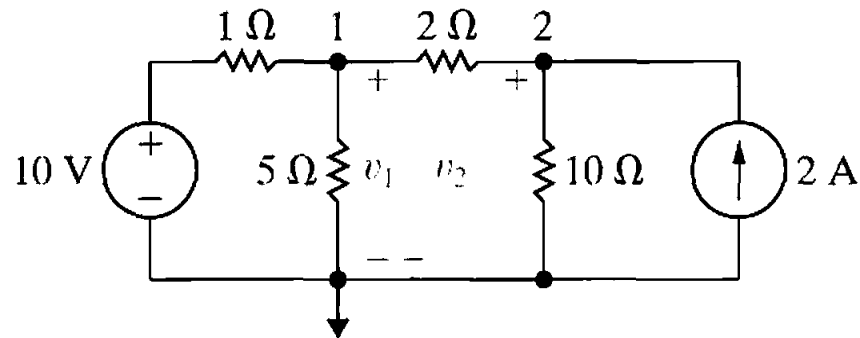
$$\frac{v_1 - 10}{1} + \frac{v_1}{5} + \frac{v_1 - v_2}{2} = 0.$$





$$\frac{v_2 - v_1}{2} + \frac{v_2}{10} - 2 = 0.$$

$$v_1 = \frac{100}{11} = 9.09 \text{ V}$$



$$v_2 = \frac{120}{11} = 10.91 \text{ V.}$$

# 7. Nodal Analysis

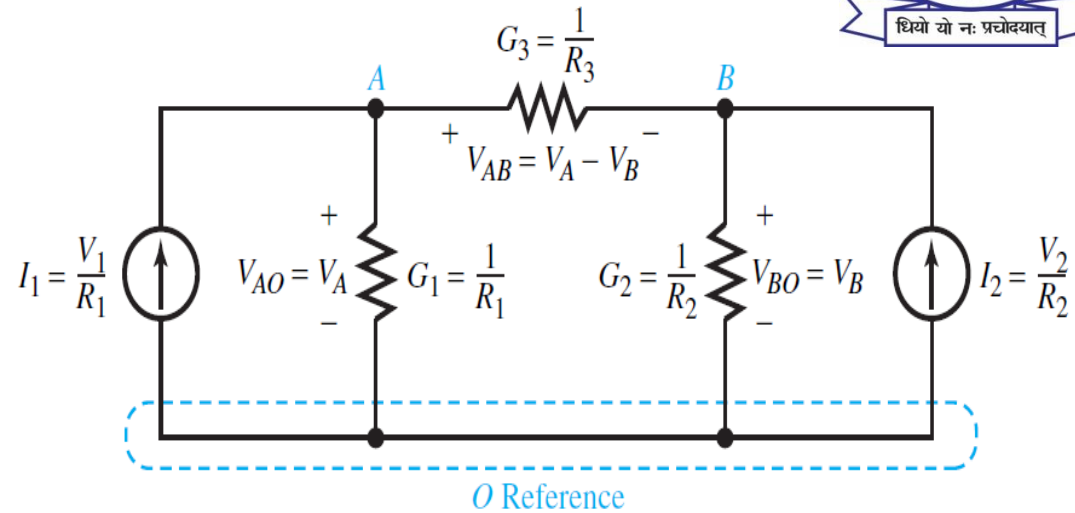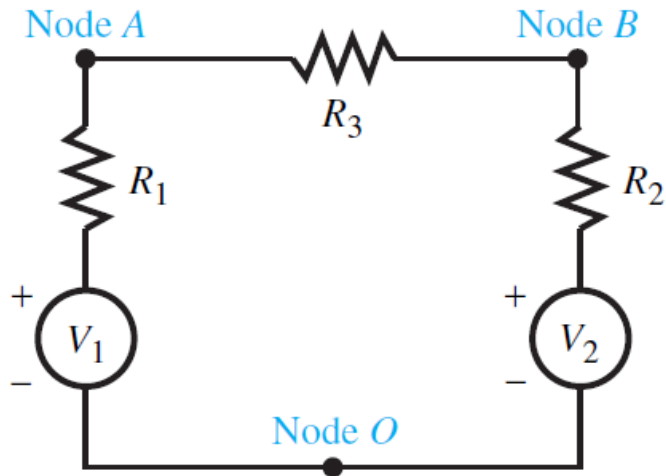

$$\begin{array}{ccccccc}
 G_{11} V_1 & - & G_{12} V_2 & - & \dots & - & G_{1N} V_N = I_1 \\
 -G_{21} V_1 & + & G_{22} V_2 & - & \dots & - & G_{2N} V_N = I_2 \\
 & & \vdots & & & & \vdots \\
 -G_{N1} V_1 & - & G_{N2} V_2 & - & \dots & + & G_{NN} V_N = I_N
 \end{array}$$

## 7. Nodal Analysis – Example

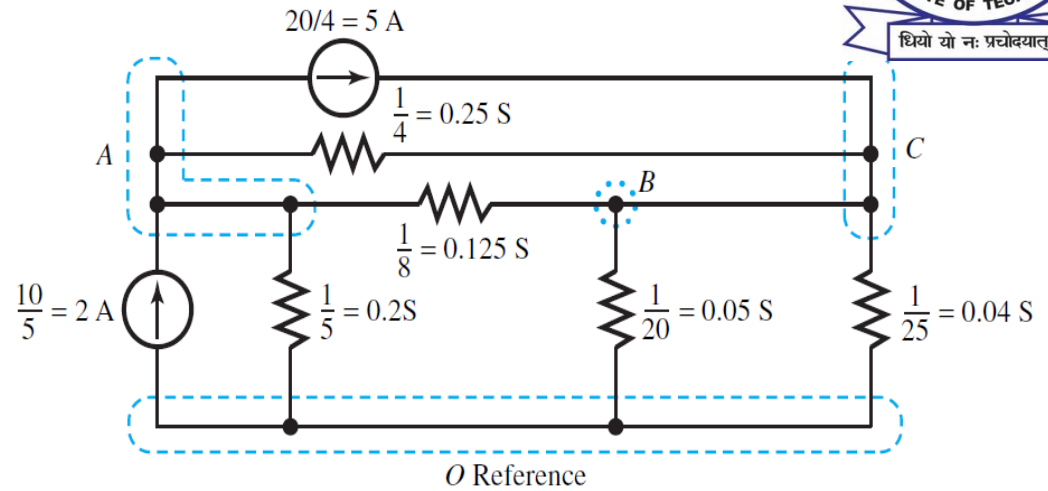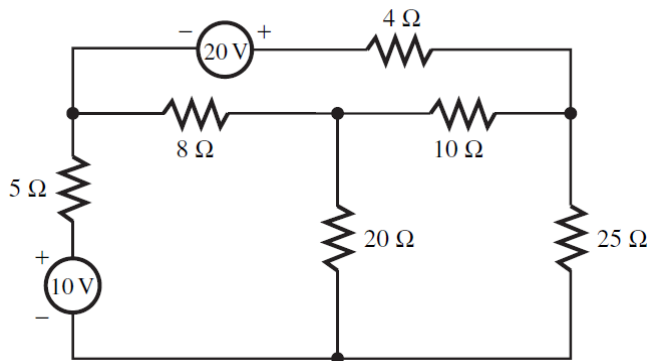

$$\text{Node A: } (0.2 + 0.125 + 0.25)V_A - 0.125V_B - 0.25V_C = 2 - 5 = -3$$

$$\text{Node B: } -0.125V_A + (0.125 + 0.05 + 0.1)V_B - 0.1V_C = 0$$

$$\text{Node C: } -0.25V_A - 0.1V_B + (0.25 + 0.1 + 0.04)V_C = 5$$


$$0.575 V_A - 0.125 V_B - 0.25 V_C = -3$$

$$-0.125 V_A + 0.275 V_B - 0.1 V_C = 0$$

$$-0.25 V_A - 0.1 V_B + 0.39 V_C = 5$$

$$V_A = 4.34 \text{ V}; \quad V_B = 8.43 \text{ V}; \quad V_C = 17.77 \text{ V}$$

## 7. Nodal Analysis – Example

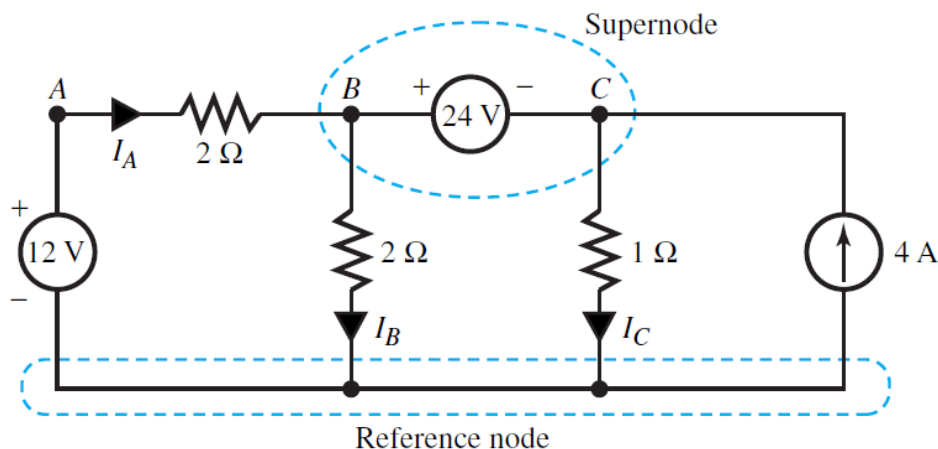

$$V_B - V_C = 24 \text{ V}$$

$$I_A - I_B - I_C + 4 = 0 \quad \text{or} \quad \frac{12 - V_B}{2} - \frac{V_B}{2} - \frac{V_C}{1} + 4 = 0$$

$$V_B + V_C = 10$$



$$V_B = 17 \text{ V} \quad \text{and} \quad V_C = -7 \text{ V}$$

$$I_A = \frac{12 - V_B}{2} = \frac{12 - 17}{2} = -2.5 \text{ A}$$

$$I_B = \frac{V_B}{2} = \frac{17}{2} = 8.5 \text{ A}$$


$$I_C = \frac{V_C}{1} = \frac{-7}{1} = -7 \text{ A}$$

# 7. Mesh current Analysis

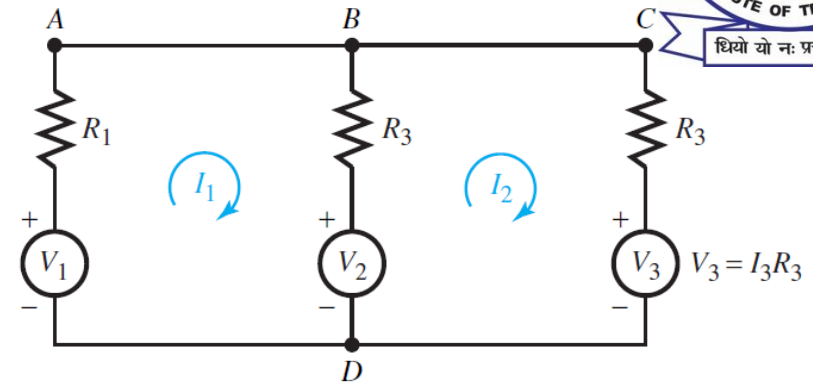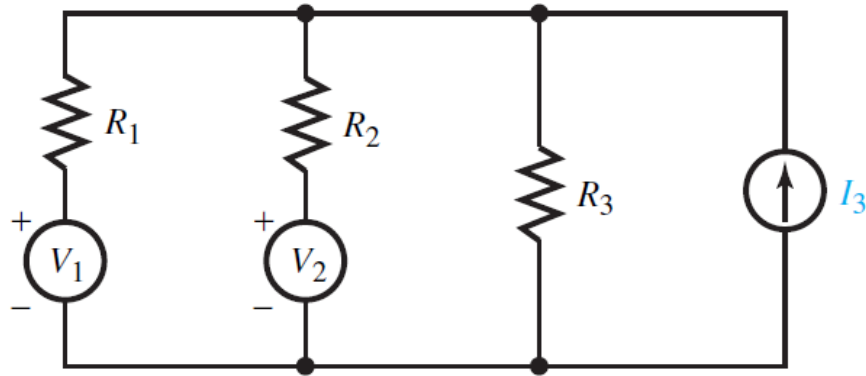

$$\begin{array}{ccccccc}
 R_{11}I_1 & - & R_{12}I_2 & - & \dots & - & R_{1N}I_N & = & V_1 \\
 -R_{21}I_1 & + & R_{22}I_2 & - & \dots & - & R_{2N}I_N & = & V_2 \\
 & \vdots & & & & & & \vdots & \\
 -R_{N1}I_1 & - & R_{N2}I_2 & - & \dots & + & R_{NN}I_N & = & V_N
 \end{array}$$

## 7. Mesh current Analysis -Example

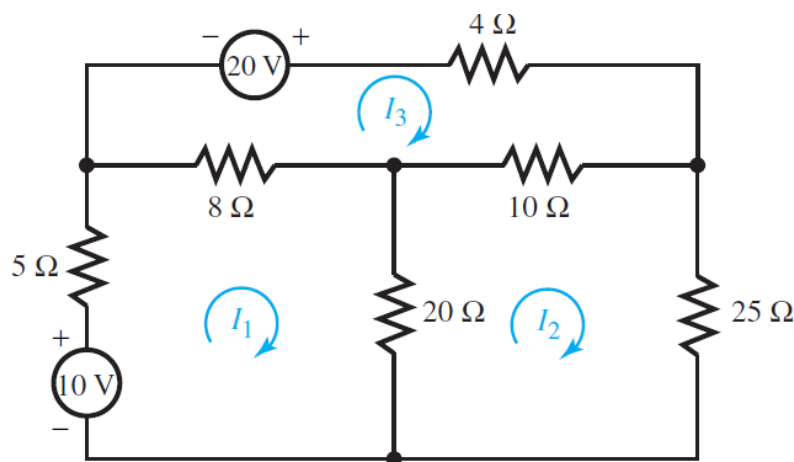

Loop 1 with mesh current  $I_1$ :  $(5 + 8 + 20)I_1 - 20I_2 - 8I_3 = 10$

Loop 2 with mesh current  $I_2$ :  $-20I_1 + (20 + 10 + 25)I_2 - 10I_3 = 0$

Loop 3 with mesh current  $I_3$ :  $-8I_1 - 10I_2 + (4 + 10 + 8)I_3 = 20$

$$33I_1 - 20I_2 - 8I_3 = 10$$


$$-20I_1 + 55I_2 - 10I_3 = 0$$

$$-8I_1 - 10I_2 + 22I_3 = 20$$

$$I_1 = 1.132 \text{ A}; \quad I_2 = 0.711 \text{ A}; \quad I_3 = 1.645 \text{ A}$$



## 7. Mesh current Analysis -Example

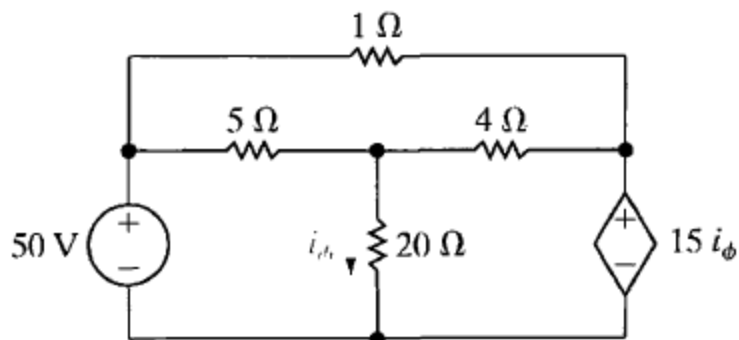


$$50 = 5(i_1 - i_2) + 20(i_1 - i_3),$$

$$0 = 5(i_2 - i_1) + 1i_2 + 4(i_2 - i_3),$$

$$0 = 20(i_3 - i_1) + 4(i_3 - i_2) + 15i_\phi.$$

$$i_\phi = i_1 - i_3,$$

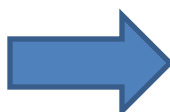

$$50 = 25i_1 - 5i_2 - 20i_3,$$

$$0 = -5i_1 + 10i_2 - 4i_3,$$


$$0 = -5i_1 - 4i_2 + 9i_3.$$



$$i_2 = 26 \text{ A},$$

$$i_3 = 28 \text{ A}.$$

## 7. Mesh current Analysis –Home work

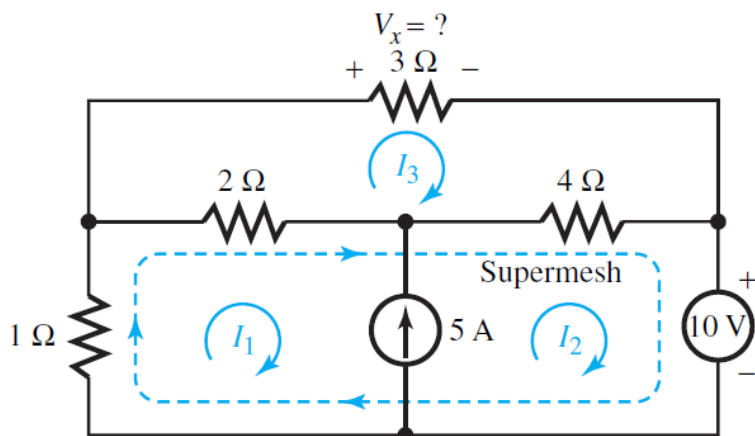

$$I_2 - I_1 = 5$$

$$1I_1 + 2(I_1 - I_3) + 4(I_2 - I_3) + 10 = 0$$


KVL equation for mesh 3

$$3I_3 + 4(I_3 - I_2) + 2(I_3 - I_1) = 0$$
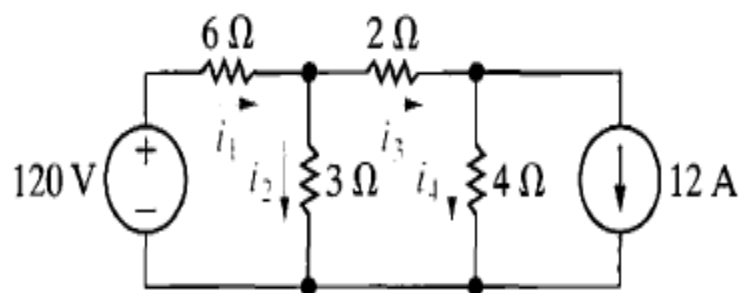
# 8. Super position theorem

$$f(Kx) = Kf(x) \quad (\text{homogeneity})$$

$$f(x_1 + x_2) = f(x_1) + f(x_2) \quad (\text{additivity})$$




$$i_1 = i'_1 + i''_1 = 15 + 2 = 17 \text{ A},$$

$$i_2 = i'_2 + i''_2 = 10 - 4 = 6 \text{ A},$$

$$i_3 = i'_3 + i''_3 = 5 + 6 = 11 \text{ A},$$
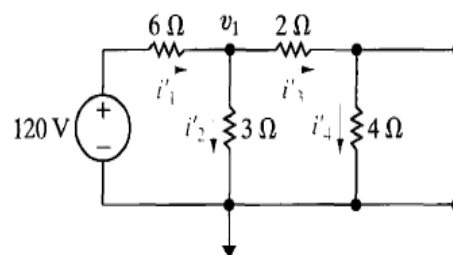
$$i_4 = i'_4 + i''_4 = 5 - 6 = -1 \text{ A}.$$




$$\frac{v_1 - 120}{6} + \frac{v_1}{3} + \frac{v_1}{2 + 4} = 0,$$

$$v_1 = 30 \text{ V}.$$

$$i'_1 = \frac{120 - 30}{6} = 15 \text{ A},$$

$$i'_2 = \frac{30}{3} = 10 \text{ A},$$
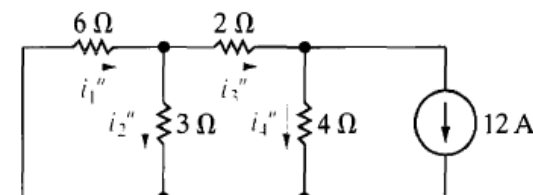
$$i'_3 = i'_4 = \frac{30}{6} = 5 \text{ A}.$$



$$\frac{v_3}{3} + \frac{v_3}{6} + \frac{v_3 - v_4}{2} = 0,$$

$$\frac{v_4 - v_3}{2} + \frac{v_4}{4} + 12 = 0.$$


$$i''_1 = \frac{-v_3}{6} = \frac{12}{6} = 2 \text{ A}$$

$$i''_2 = \frac{v_3}{3} = \frac{-12}{3} = -4 \text{ A}.$$


$$i''_3 = \frac{v_3 - v_4}{2} = \frac{-12 + 24}{2} = 6 \text{ A}$$

$$i''_4 = \frac{v_4}{4} = \frac{-24}{4} = -6 \text{ A}$$

## 8. Super position theorem- example

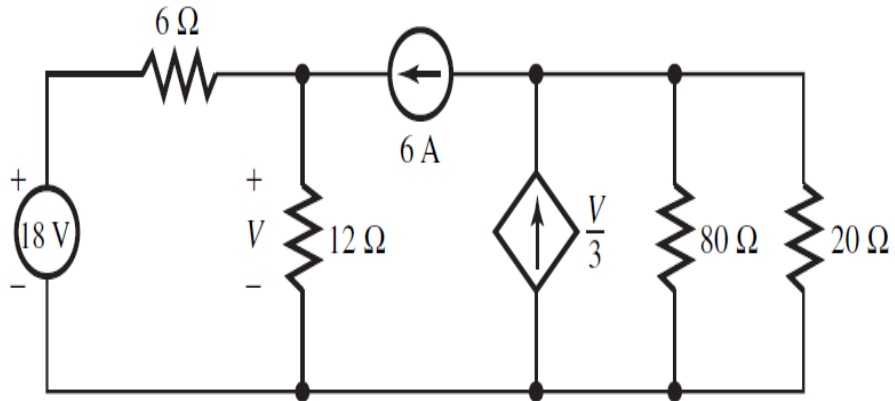


# 9. Star-delta and delta-star

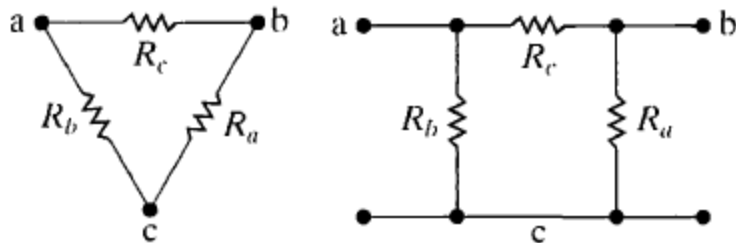

$$R_{ab} = \frac{R_c(R_a + R_b)}{R_a + R_b + R_c} = R_1 + R_2,$$

$$R_{bc} = \frac{R_a(R_b + R_c)}{R_a + R_b + R_c} = R_2 + R_3,$$
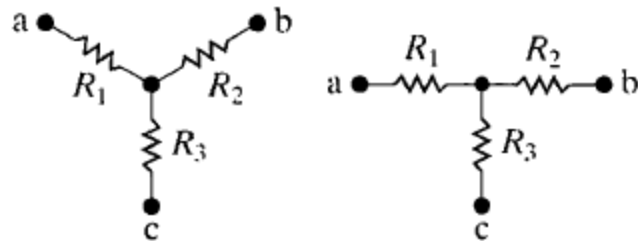
$$R_{ca} = \frac{R_b(R_c + R_a)}{R_a + R_b + R_c} = R_1 + R_3.$$



$\Delta$ -to-Y

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c},$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c},$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}.$$


Y-to- $\Delta$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1},$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2},$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}.$$


## 9. Star- Delta transform Example

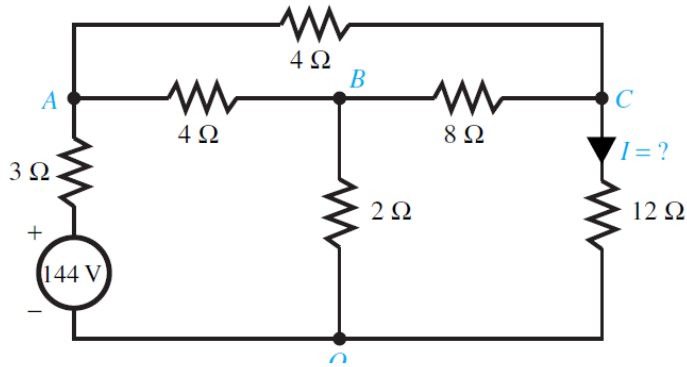

$$R_1 = \frac{4 \times 4}{4 + 8 + 4} = 1 \Omega$$

$$R_2 = \frac{4 \times 8}{4 + 8 + 4} = 2 \Omega$$


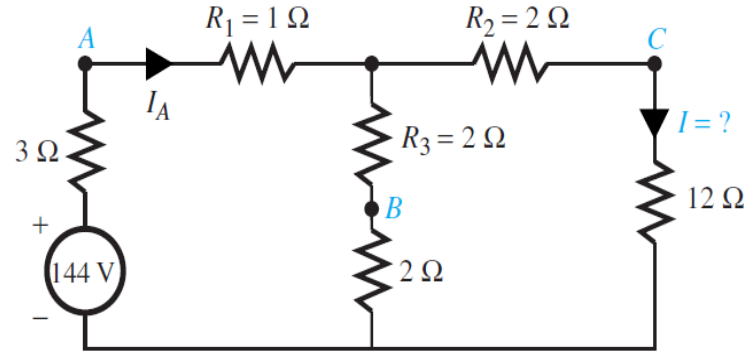
$$R_3 = \frac{4 \times 8}{4 + 8 + 4} = 2 \Omega$$



$$I_A = \frac{144}{(3 + 1) + (4 \parallel 12)} = \frac{81}{4} \text{ A}$$

$$I = \frac{81}{4} \times \frac{4}{18} = \frac{9}{2} = 4.5 \text{ A}$$

# 10. The Thevenin and norton theorem

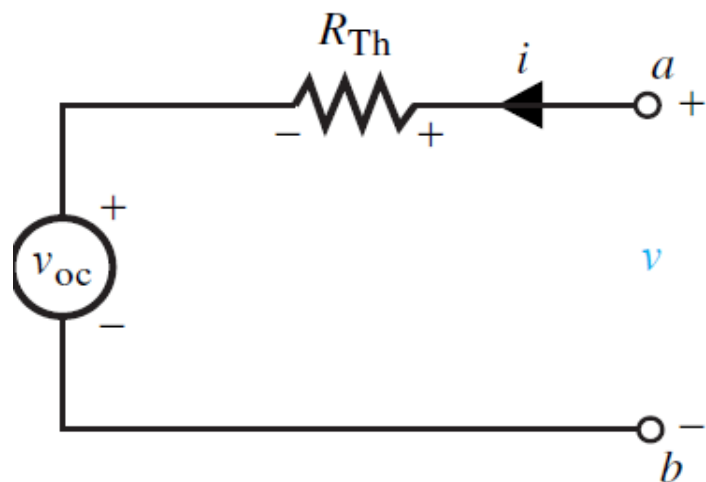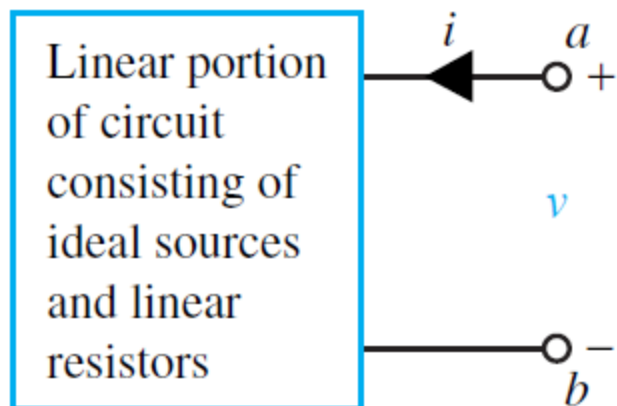


**Thevenin Equivalent**

$$v = R_{Th}i + v_{oc}$$

$$R_{Th} = v/i|_{v_{oc}=0}$$


$$v_{oc} = v|i=0$$
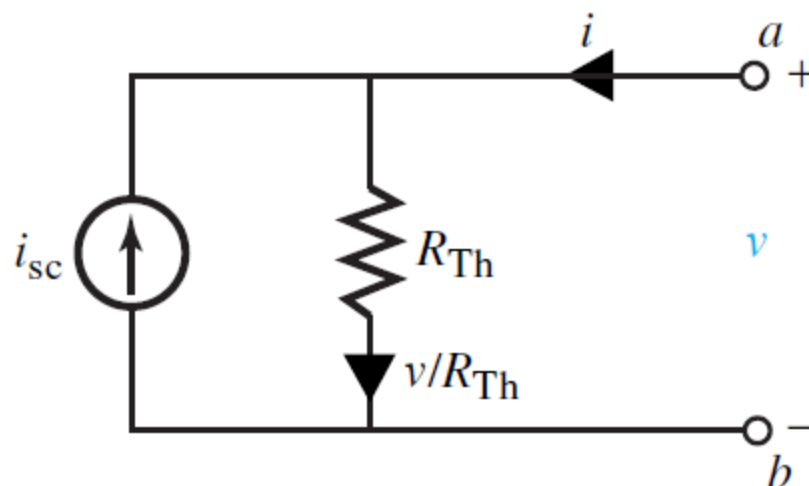
$$i = \frac{v}{R_{Th}} - \frac{v_{oc}}{R_{Th}} = \frac{v}{R_{Th}} - i_{sc}$$




**Norton Equivalent**

## 10. The Thevenin theorem - example

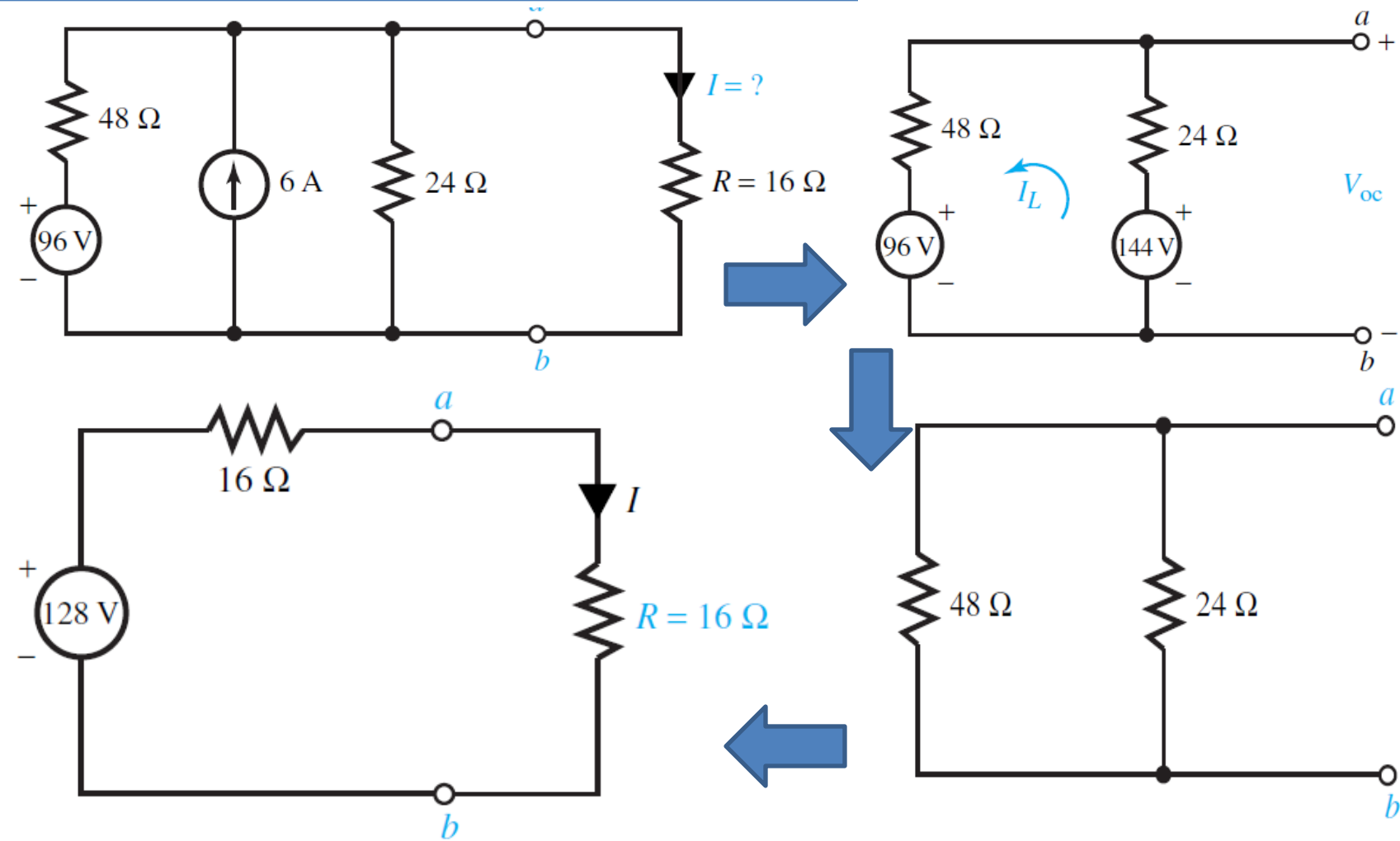




## 10. The Thevenin theorem - example

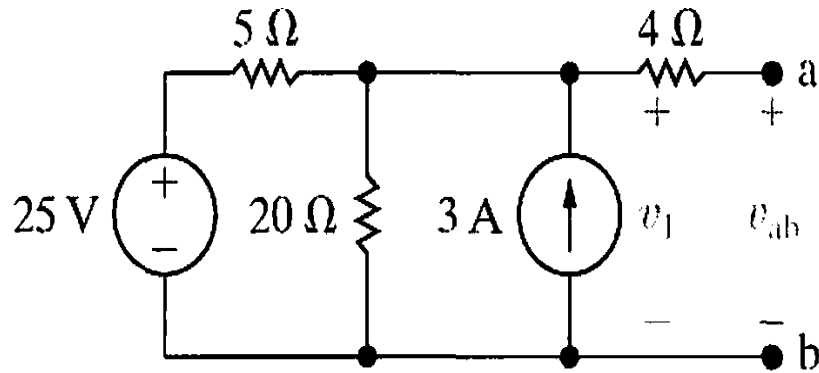

$$\frac{v_1 - 25}{5} + \frac{v_1}{20} - 3 = 0.$$


$$v_1 = 32 \text{ V.}$$

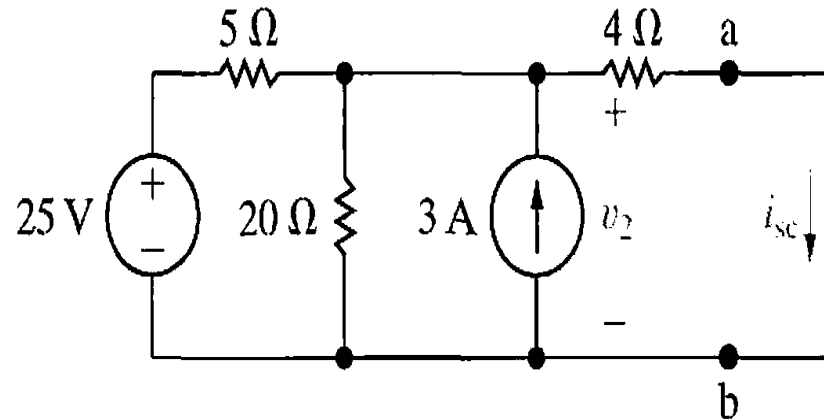

$$\frac{v_2 - 25}{5} + \frac{v_2}{20} - 3 + \frac{v_2}{4} = 0.$$


$$v_2 = 16 \text{ V.}$$

$$i_{sc} = \frac{16}{4} = 4 \text{ A.}$$

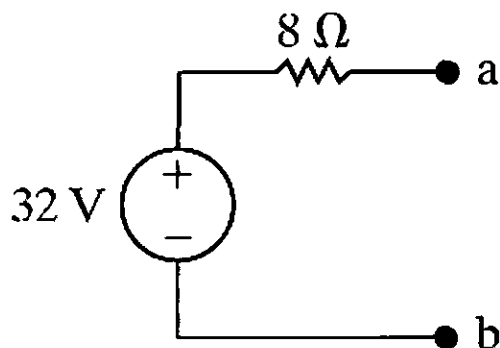


$$R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{32}{4} = 8 \Omega.$$

## 10. The Norton theorem - example

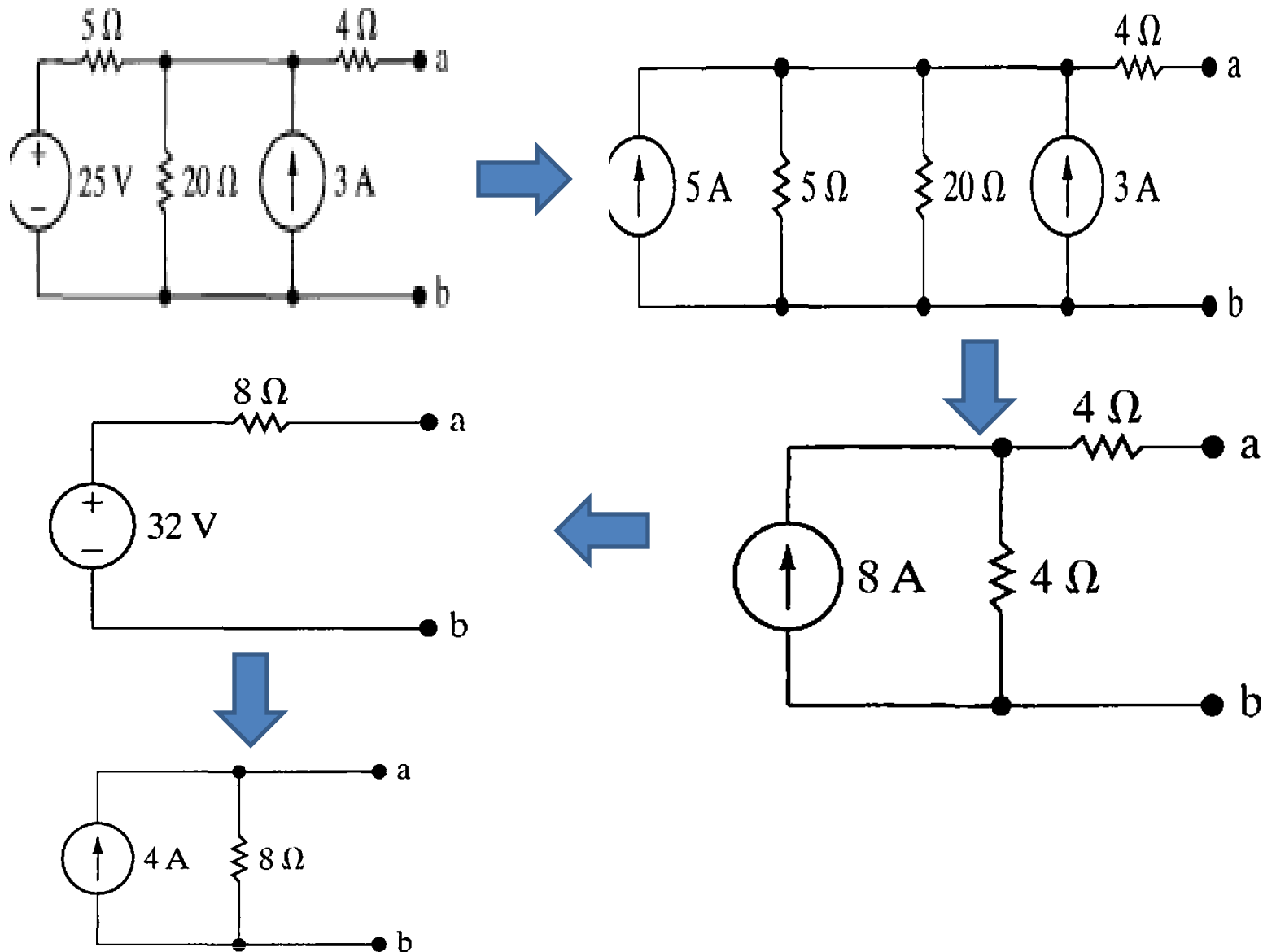

# 11. Maximum power transfer theorem

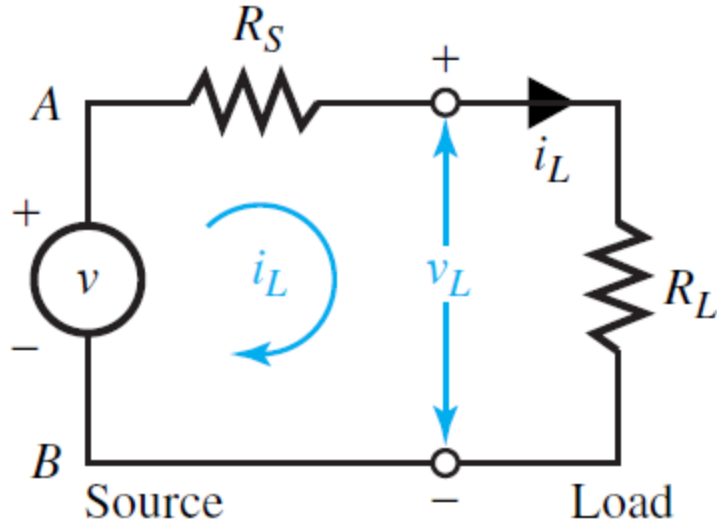

$$P_L = i_L^2 R_L$$

$$i_L = \frac{v}{R_S + R_L}$$

$$P_L = \frac{v^2}{(R_S + R_L)^2} R_L$$

$$\frac{dP_L}{dR_L} = \frac{v^2(R_L + R_S)^2 - 2v^2 R_L(R_L + R_S)}{(R_L + R_S)^4} = 0$$


$$(R_L + R_S)^2 - 2R_L(R_L + R_S) = 0$$

$$R_L = R_S$$



## 12. Capacitor Principle



$$i = C \frac{dv}{dt}$$


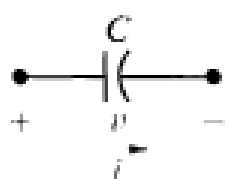

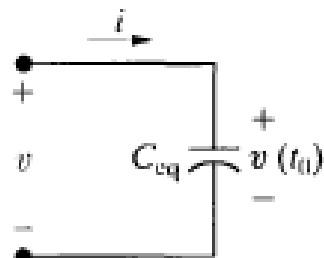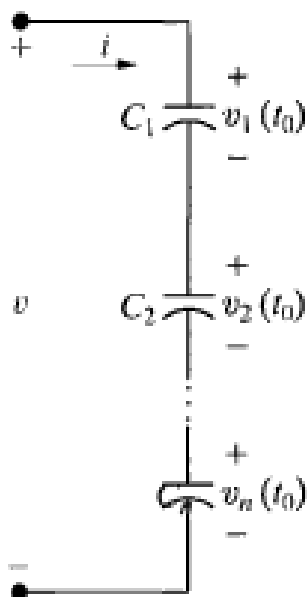
$$i dt = C dv \quad \text{or} \quad \int_{v(t_0)}^{v(t)} dx = \frac{1}{C} \int_{t_0}^t i d\tau, \quad p = vi = Cv \frac{dv}{dt}$$




$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$
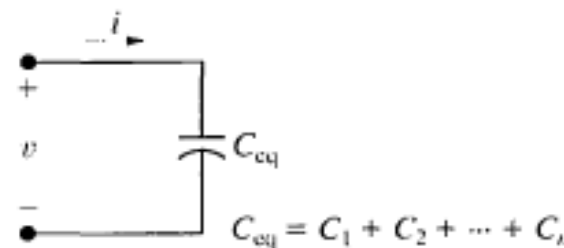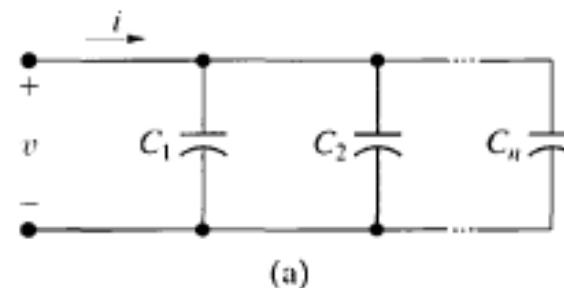
$$v(t_0) = v_1(t_0) + v_2(t_0) + \dots + v_n(t_0)$$




## 12. Natural response of RC circuit

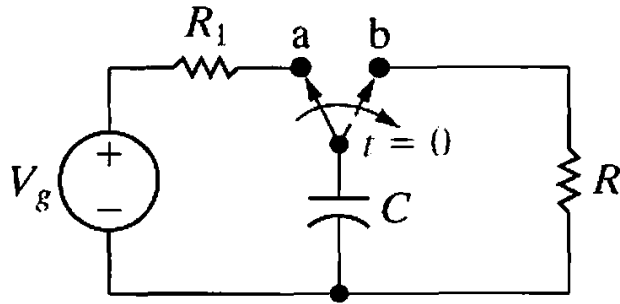

$$C \frac{dv}{dt} + \frac{v}{R} = 0.$$

$$v(t) = v(0)e^{-t/RC}, \quad t \geq 0.$$

$$\tau = RC.$$

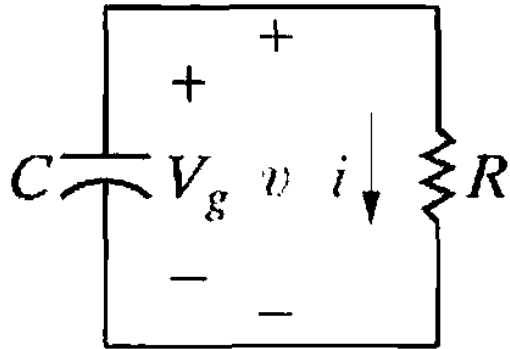


$$i(t) = \frac{v(t)}{R} = \frac{V_0}{R}e^{-t/\tau}, \quad t \geq 0^+,$$


$$p = vi = \frac{V_0^2}{R}e^{-2t/\tau}, \quad t \geq 0^+,$$

$$w = \int_0^t p \, dx = \int_0^t \frac{V_0^2}{R}e^{-2x/\tau} \, dx$$
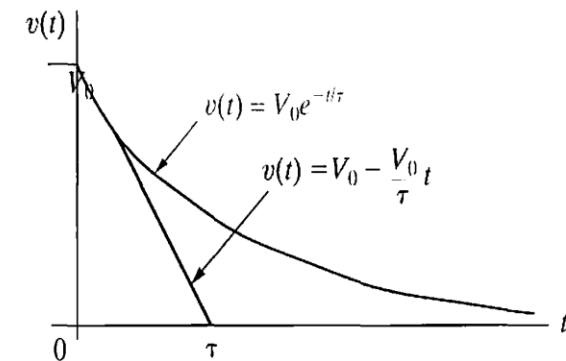
$$= \frac{1}{2}CV_0^2(1 - e^{-2t/\tau}), \quad t \geq 0.$$


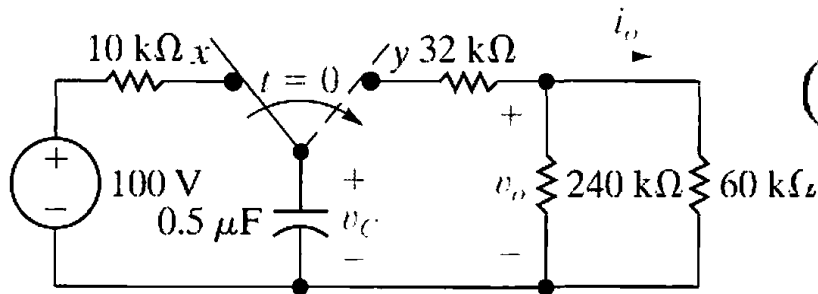
## 12. Natural response of RC circuit - example



time constant  
 $(0.5 \times 10^{-6})(80 \times 10^3)$

$$v_C(t) = 100e^{-25t} \text{ V}, \quad t \geq 0.$$


$$v_o(t) = \frac{48}{80}v_C(t) = 60e^{-25t} \text{ V}, \quad t \geq 0^+.$$

$$i_o(t) = \frac{v_o(t)}{60 \times 10^3} = e^{-25t} \text{ mA}, \quad t \geq 0^+.$$

$$p_{60\text{k}\Omega}(t) = i_o^2(t)(60 \times 10^3) = 60e^{-50t} \text{ mW}, \quad t \geq 0^+.$$


$$w_{60\text{k}\Omega} = \int_0^{\infty} i_o^2(t)(60 \times 10^3) dt = 1.2 \text{ mJ}.$$

# 13. Natural response of RL circuit

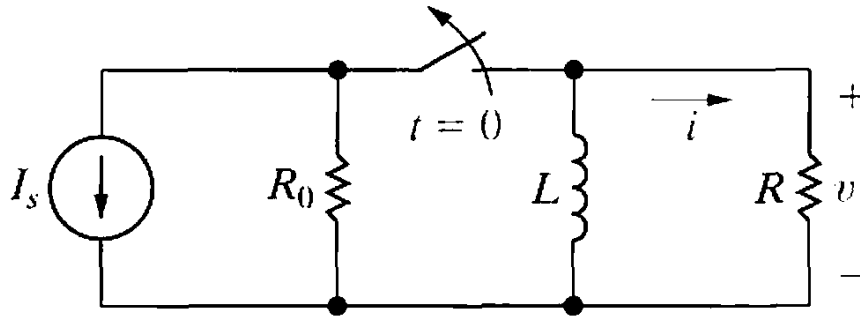

$$L \frac{di}{dt} + Ri = 0,$$

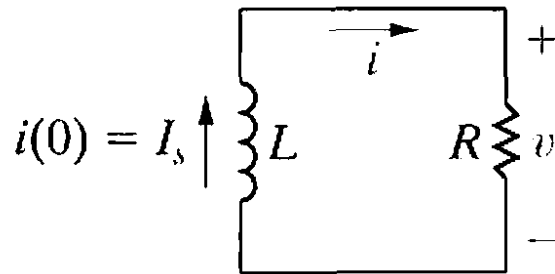
$$\frac{di}{dt} dt = -\frac{R}{L} i dt.$$




$$\frac{di}{i} = -\frac{R}{L} dt. \quad \ln \frac{i(t)}{i(0)} = -\frac{R}{L} t.$$

$$i(t) = i(0)e^{-(R/L)t}, \quad i(0^-) = i(0^+) = I_0,$$
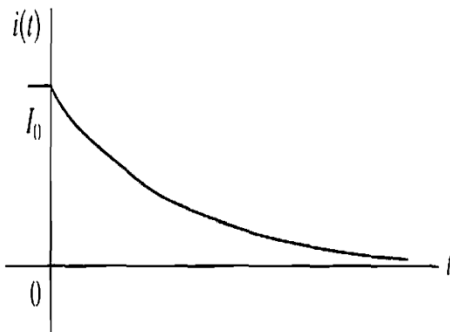
$$i(t) = I_0 e^{-(R/L)t}, \quad t \geq 0,$$



## 13. Natural response of RL circuit

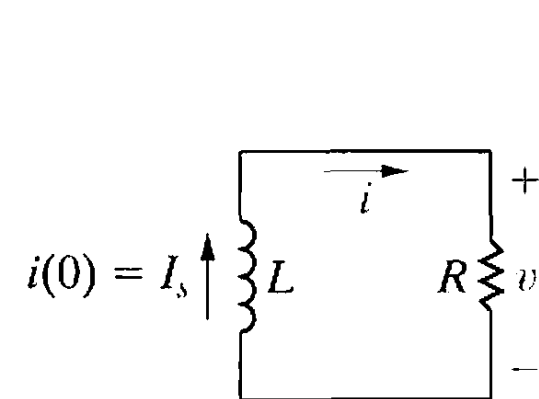

$$p = vi, \quad p = i^2 R, \quad \text{or} \quad p = \frac{v^2}{R}.$$

$$p = I_0^2 R e^{-2(R/L)t}, \quad t \geq 0^+.$$


$$w = \int_0^t p dx = \int_0^t I_0^2 R e^{-2(R/L)x} dx$$

$$= \frac{1}{2(R/L)} I_0^2 R (1 - e^{-2(R/L)t})$$

$$= \frac{1}{2} L I_0^2 (1 - e^{-2(R/L)t}), \quad t \geq 0.$$


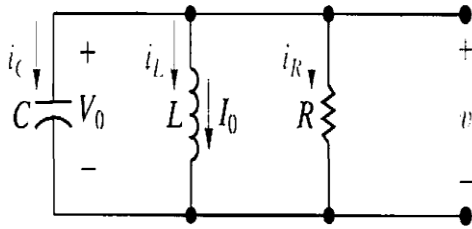
# 13. Natural response of Parallel RLC circuit



$$\frac{1}{R} \frac{dv}{dt} + \frac{v}{L} + C \frac{d^2v}{dt^2} = 0.$$

$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0.$$

$$As^2e^{st} + \frac{As}{RC}e^{st} + \frac{Ae^{st}}{LC} = 0,$$

$$Ae^{st} \left( s^2 + \frac{s}{RC} + \frac{1}{LC} \right) = 0,$$

$$s^2 + \frac{s}{RC} + \frac{1}{LC} = 0.$$

$$s_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}},$$


$$s_2 = -\frac{1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}.$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2},$$


$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2},$$

$$\alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\zeta = \frac{\alpha}{\omega_0}$$

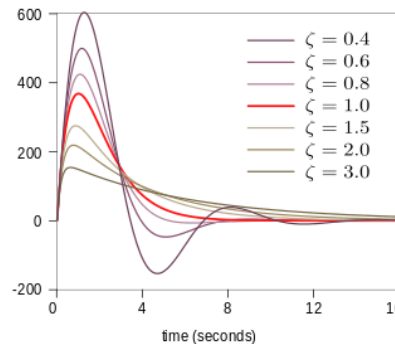

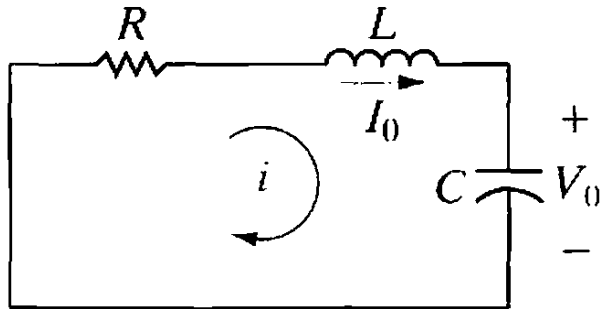
# 13. Natural response of series RLC circuit



$\omega_0^2 < \alpha^2, \omega_0^2 > \alpha^2, \text{ or } \omega_0^2 = \alpha^2,$   
overdamped, underdamped, or critically damped

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0.$$
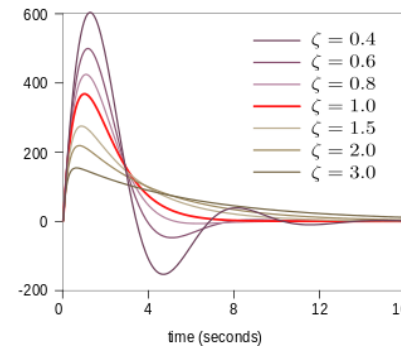
$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0.$$



$$s_{1,2} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}},$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}.$$


$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \text{ (overdamped),}$$

$$i(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t \text{ (underdamped).}$$

$$i(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t} \text{ (critically damped).}$$

$$\alpha = \frac{R}{2L} \text{ rad/s, } \omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/s.}$$


# 14. Single phase AC circuits

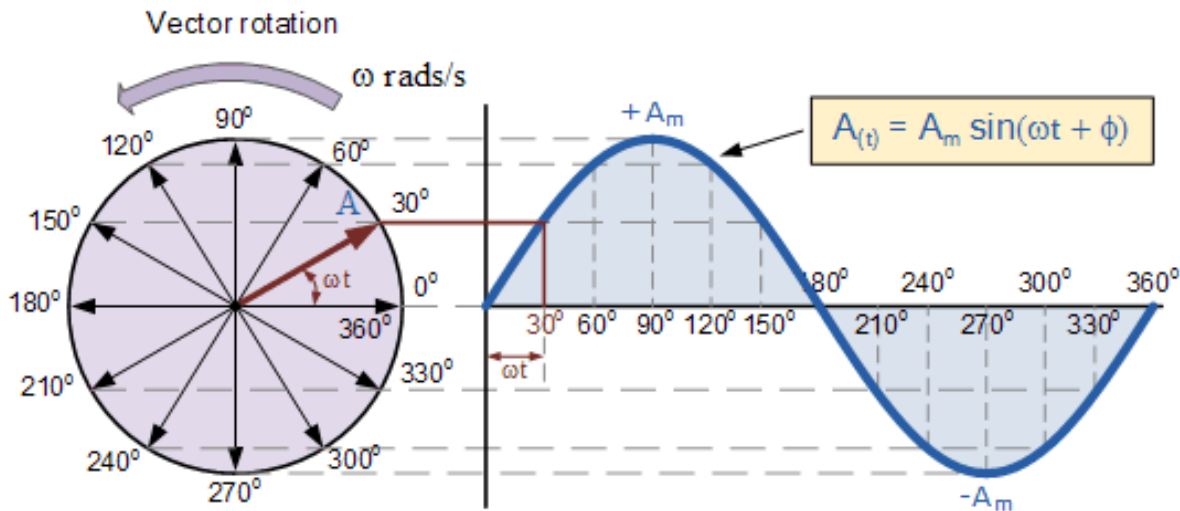


Rotating Phasor

Sinusoidal Waveform in the Time Domain

$$v(t) = V_m \sin(\omega t)$$


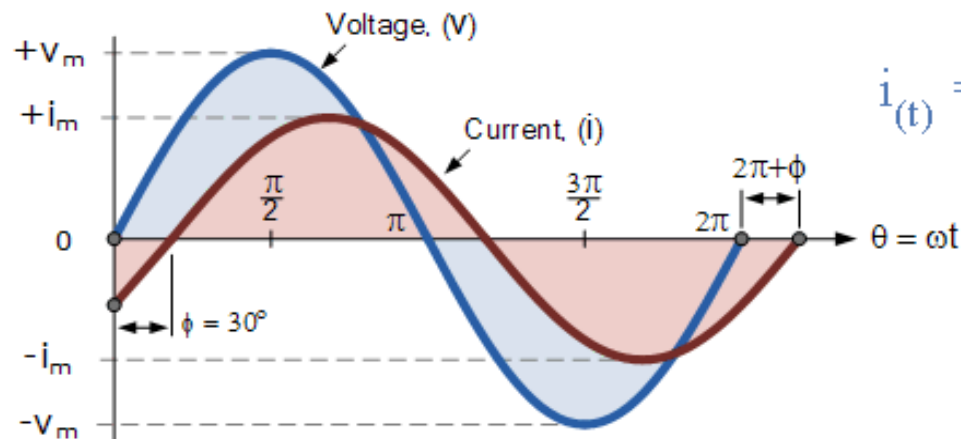


$$i(t) = I_m \sin(\omega t - \phi)$$

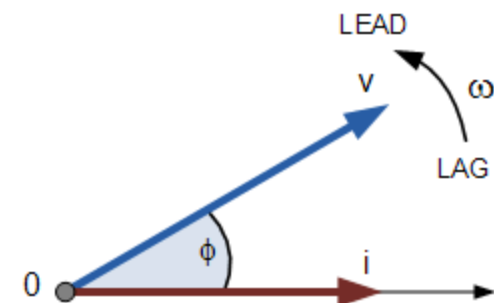


# 15. Series RL circuits

Sine wave generator


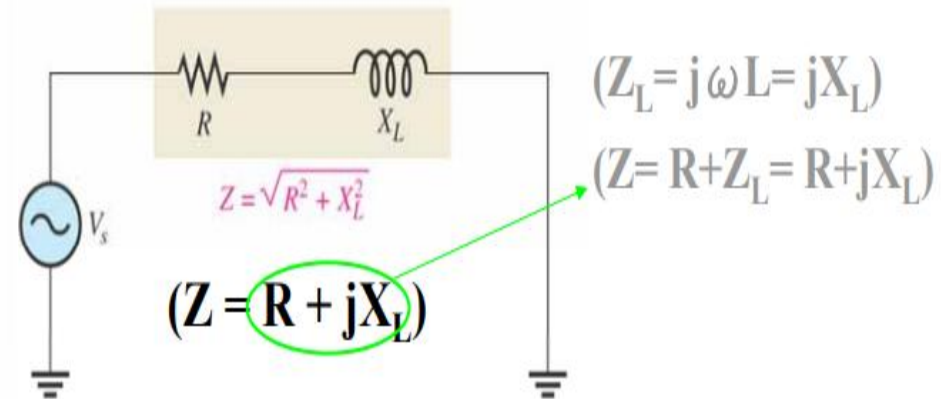
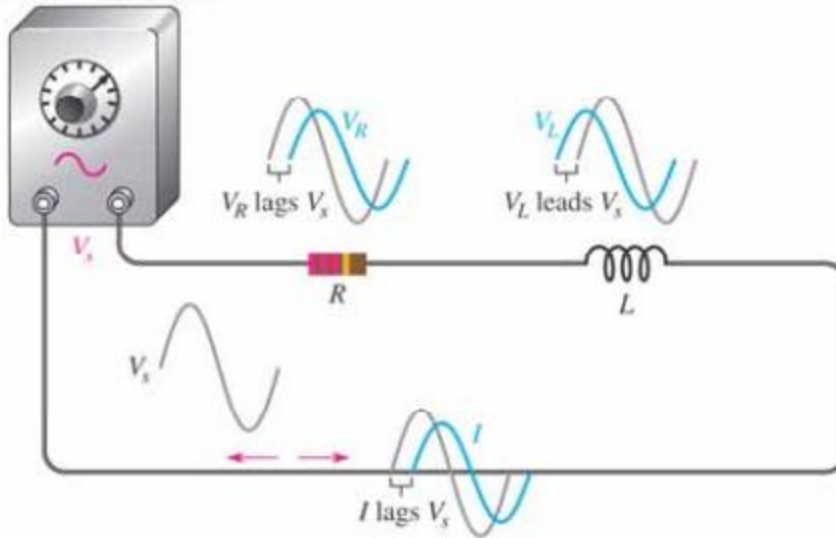


$$Z = \sqrt{R^2 + X_L^2}$$

$$\theta = \tan^{-1}(X_L/R)$$

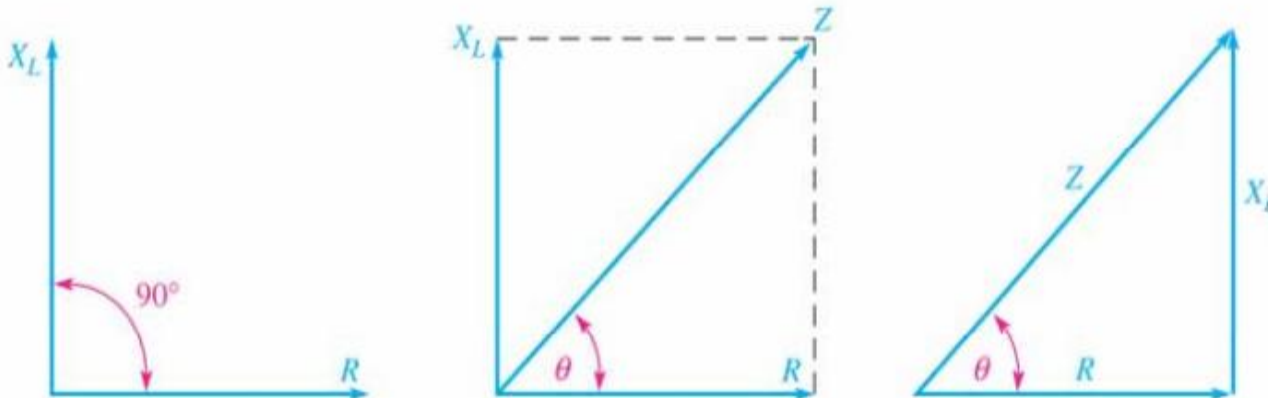

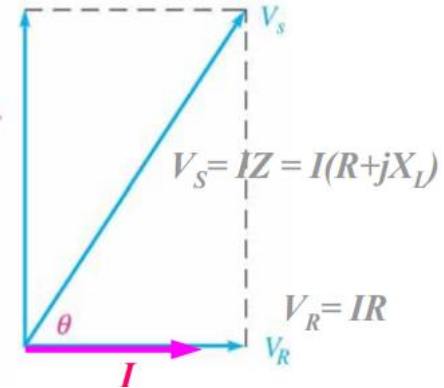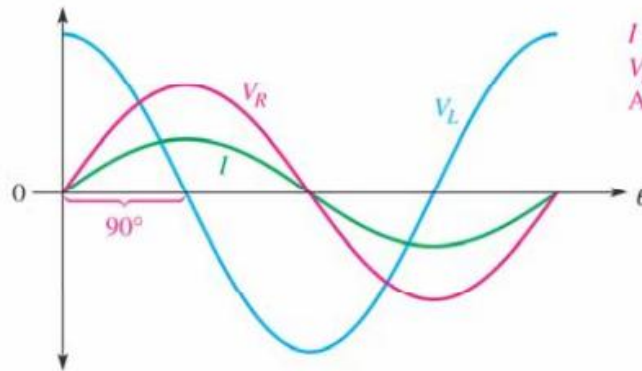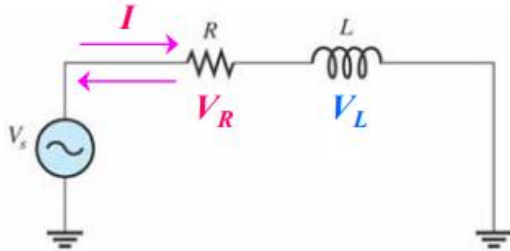
# 15. Relationship I and V in series RL circuit




$$V_S = \sqrt{V_R^2 + V_L^2}$$

$$\theta = \tan^{-1}(V_L/V_R)$$


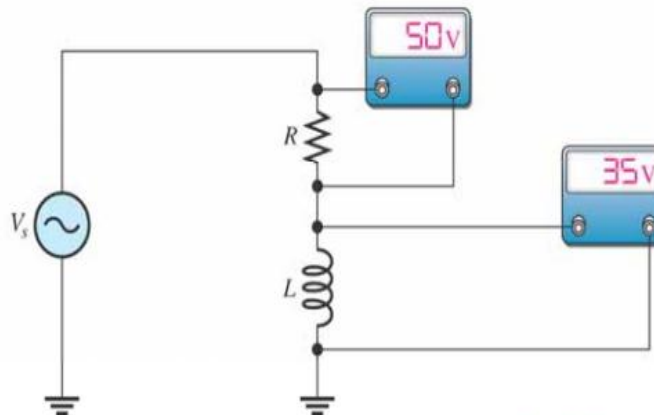


$$V_S = \sqrt{(50)^2 + (35)^2} = 61 \text{ V}$$




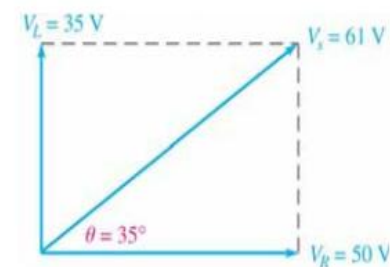
$$\theta = \tan^{-1}(35/50) = \tan^{-1}(0.7) = 35^\circ$$



# 15. Series RC circuits

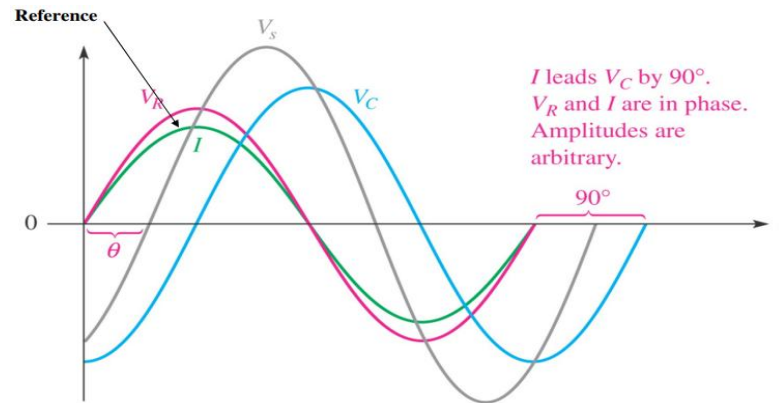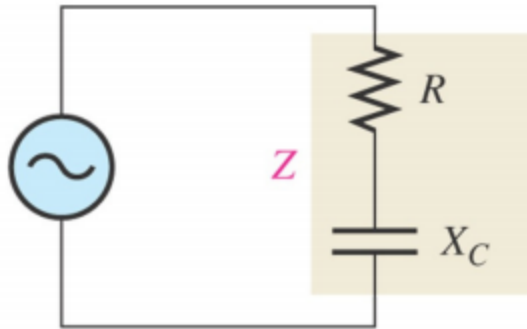


$I_t$  is the used as the Reference Wave

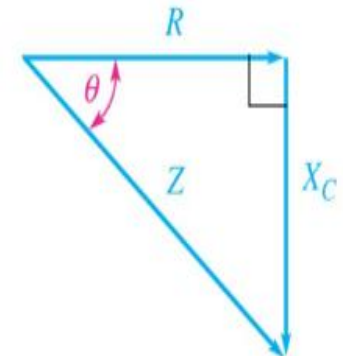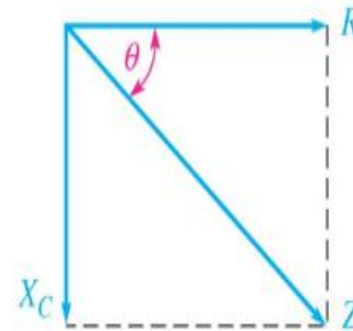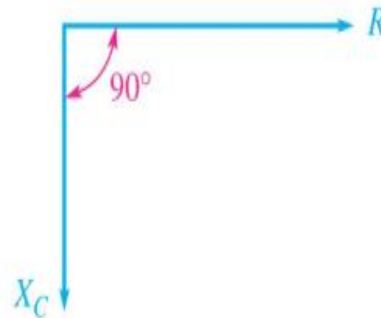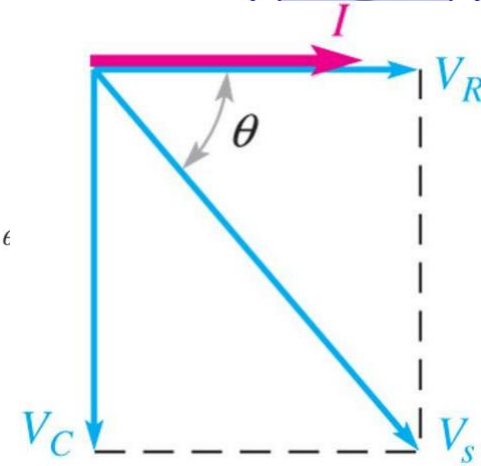

$$Z = \sqrt{R^2 + X_C^2}$$

$$\theta = \tan^{-1}(X_C/R)$$

# 15. Series RC circuits- example

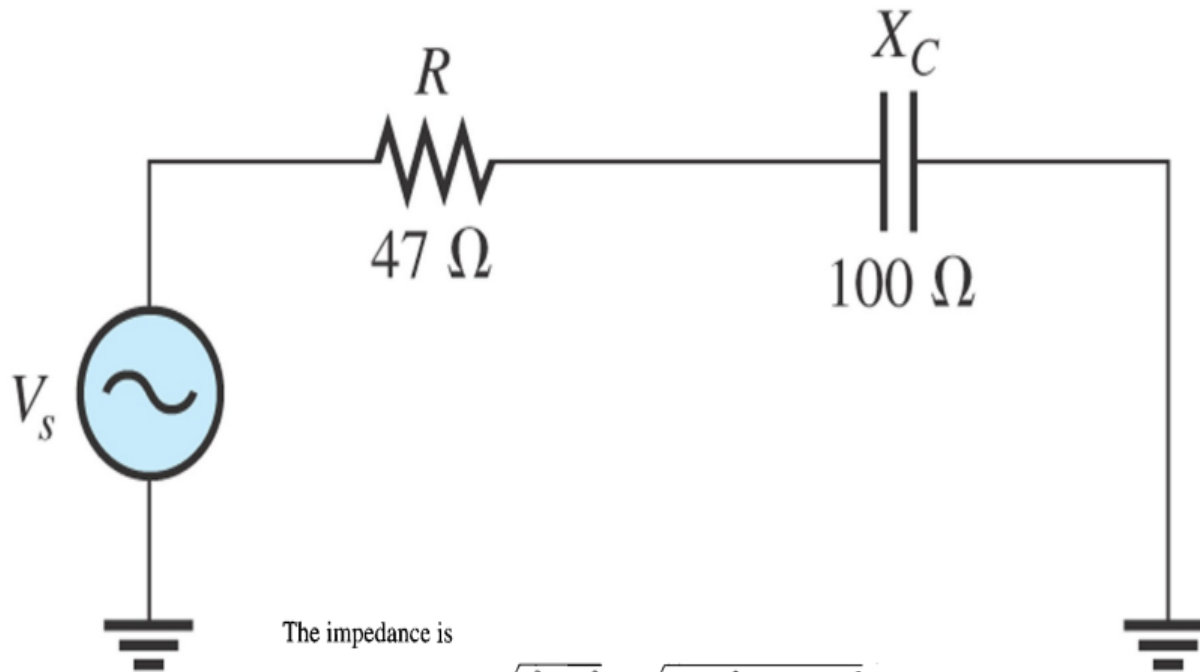


The impedance is

$$Z = \sqrt{R^2 + X_C^2} = \sqrt{(47\ \Omega)^2 + (100\ \Omega)^2} = 110\ \Omega$$


The phase angle is

$$\theta = \tan^{-1}\left(\frac{X_C}{R}\right) = \tan^{-1}\left(\frac{100\ \Omega}{47\ \Omega}\right) = \tan^{-1}(2.13) = 64.8^\circ$$

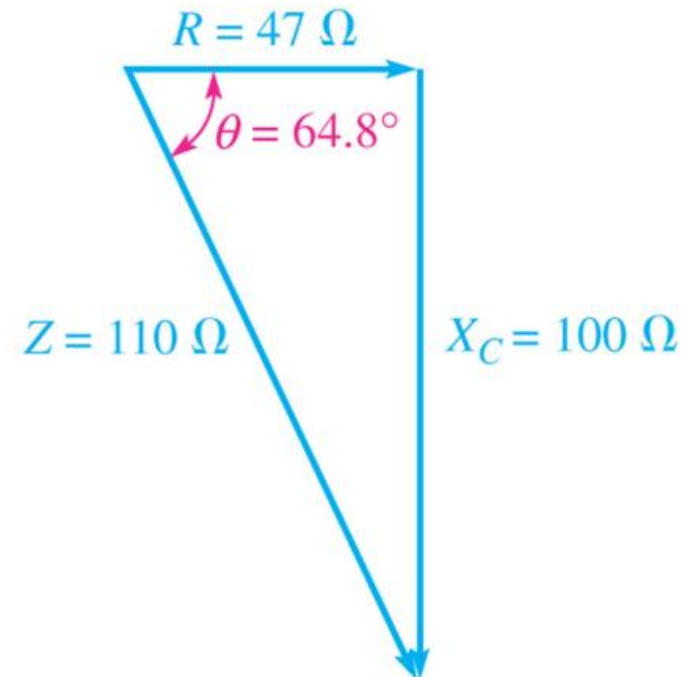The source voltage lags the current by 64.8 Degrees



# 15. Series RC circuits- example

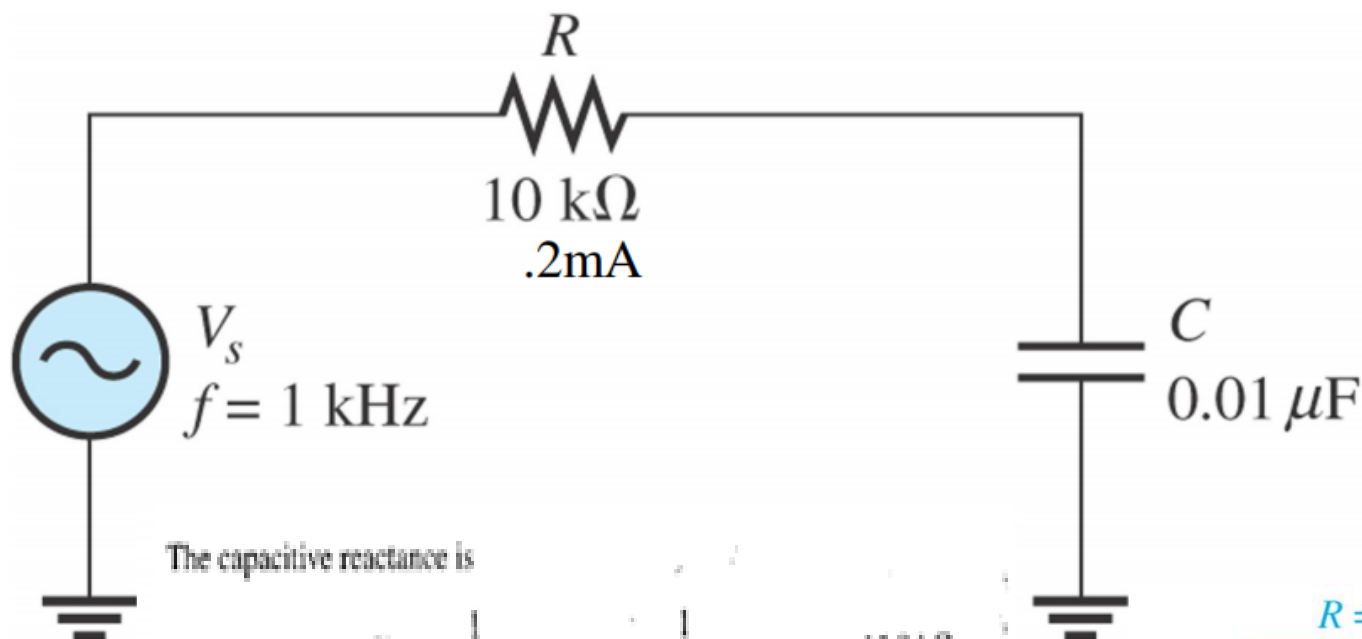

The capacitive reactance is

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(1000 \text{ Hz})(0.01 \text{ }\mu\text{F})} = 15.9 \text{ k}\Omega$$

The impedance is

$$Z = \sqrt{R^2 + X_C^2} = \sqrt{(10 \text{ k}\Omega)^2 + (15.9 \text{ k}\Omega)^2} = 18.8 \text{ k}\Omega$$

Applying Ohm's law yields

$$V_s = IZ = (0.2 \text{ mA})(18.8 \text{ k}\Omega) = 3.76 \text{ V}$$

The phase angle is

$$\theta = \tan^{-1}\left(\frac{X_C}{R}\right) = \tan^{-1}\left(\frac{15.9 \text{ k}\Omega}{10 \text{ k}\Omega}\right) = 57.8^\circ$$

