


# Magnetic Coupled Circuits

By

Bibhu Prasad Padhy
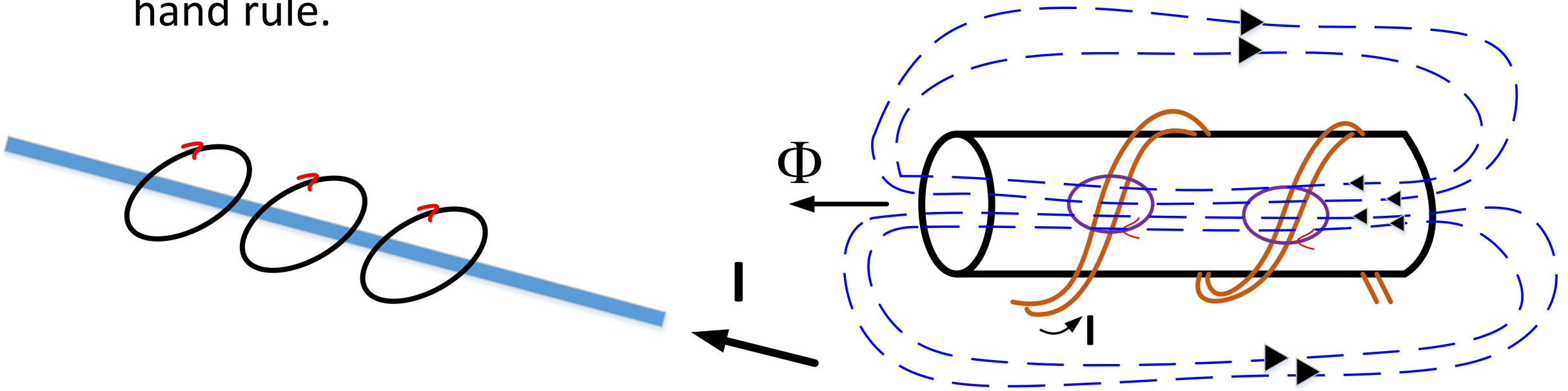
# Introduction

- Magnetic flux produced around a conductor carrying AC and DC currents.
- The direction of the flux can be determined by the “Fleming’s” right hand rule.



Flux produced by a current carrying conductor


# Mutual Inductance

- Let  $i$  is the current flowing through the conductor and  $\Phi$  is the average flux produced in the direction normal to the cross-section of the coil.
- Assume  $N$  is the numbers turns in the coil.
- The flux linkage is defined as,  $\lambda = N\Phi$
- The inductance of the coil is defined as,  $L = \frac{\lambda}{i} = \frac{N\Phi}{i}$
- The relation between the terminal of the voltage and current for an inductor is given as,

$$v = \frac{d\lambda}{dt} = N \frac{d\Phi}{dt} = L \frac{di}{dt}$$
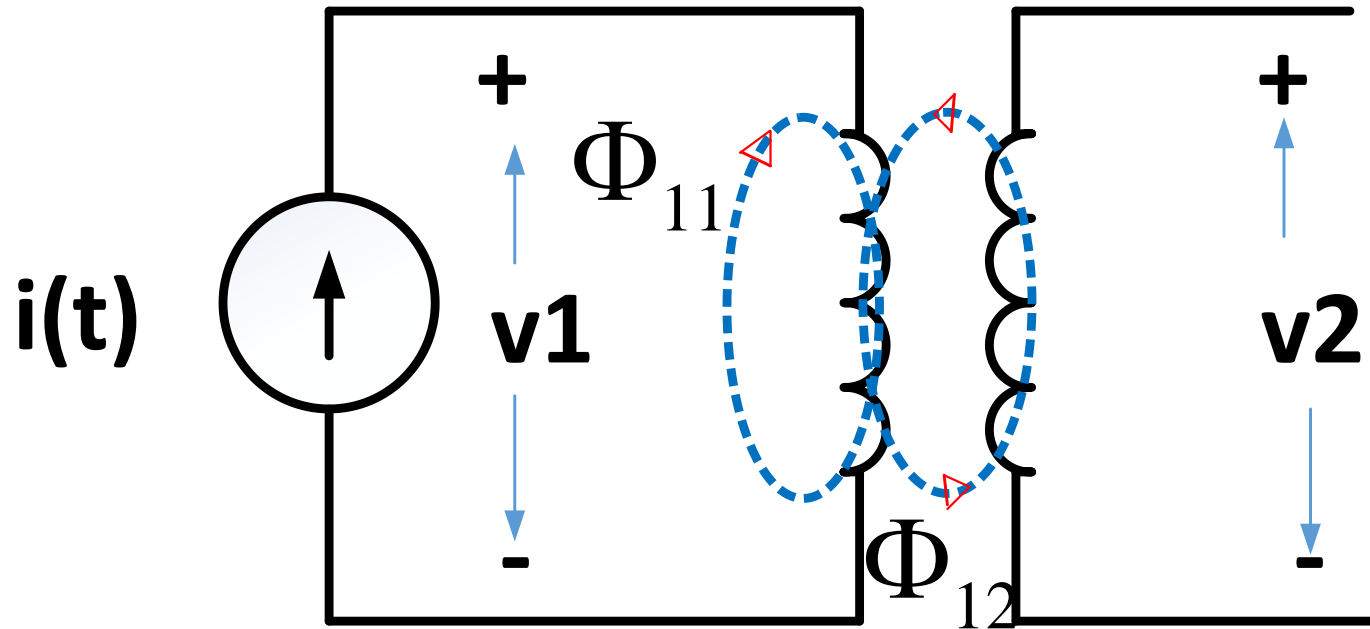
# Mutual Inductance (Contd..)

- The inductance presented above equation is the “ self-inductance” of the coil.
- Let us consider another coil in the vicinity of the inductor.



# Mutual Inductance (Contd..)

- Let two coils of self-inductance  $L_1$  and  $L_2$  placed in the close proximity of each other.
- Coil-1 has  $N_1$  number of turns and coil-2 has  $N_2$  turns.
- The total flux,

$$\Phi_1 = \Phi_{11} + \Phi_{12}$$

- The total flux links with coil-1. Hence,

$$\begin{aligned} v_1 &= N_1 \frac{d\Phi_1}{dt} = \frac{d}{dt} (N_1 \Phi_1) \\ &= \frac{d}{dt} (L_1 i_1) = L_1 \frac{di_1}{dt} \end{aligned}$$

# Mutual Inductance (Contd..)


- The flux  $\Phi_{12}$  is only links with coil-2. Hence,

$$\begin{aligned}v_2 &= N_2 \frac{d\Phi_{12}}{dt} = N_2 \frac{d\Phi_{12}}{di_1} \cdot \frac{di_1}{dt} \\&= M_{21} \frac{di_1}{dt}\end{aligned}$$



- Where  $M_{21} = N_2 \frac{d\Phi_{12}}{di_1}$
- $M_{21}$  is called the mutual inductance of coil-2 with respect to coil-1
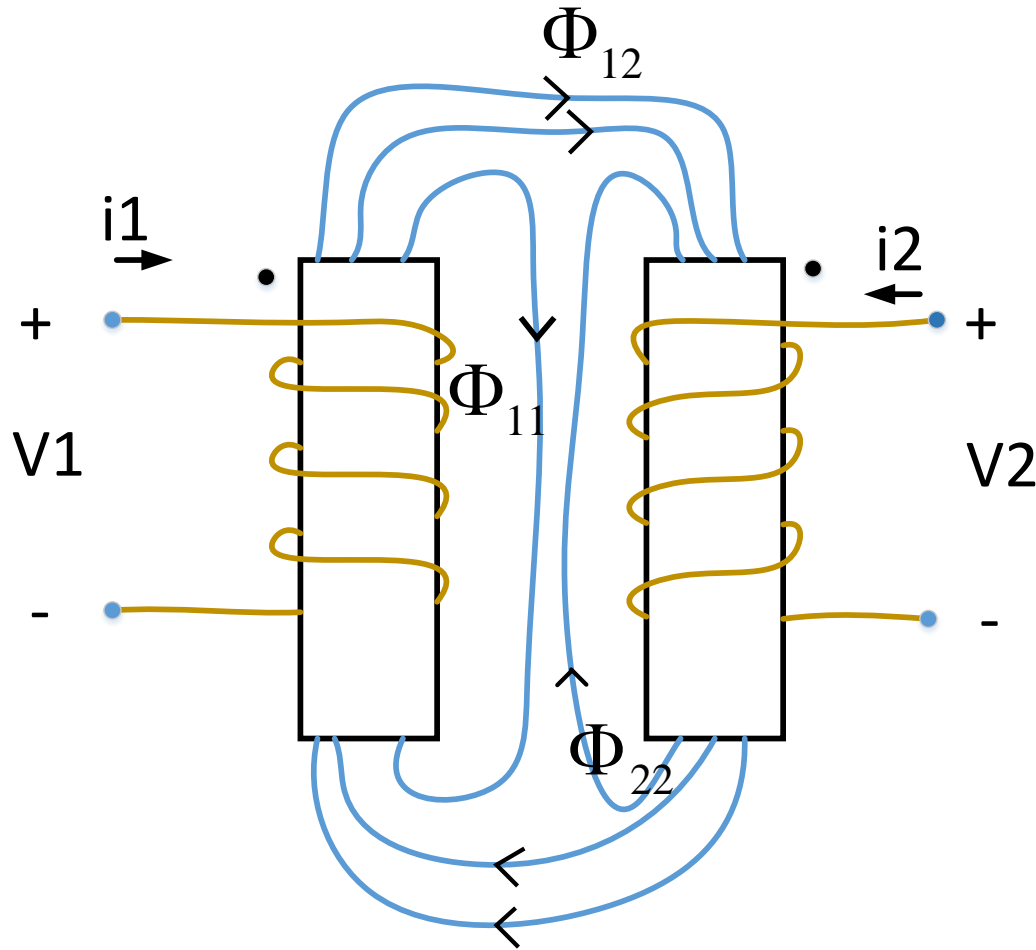
# Dot Convention

- Dots are used to mark the polarities of voltages





# Dot Convention (Contd..)

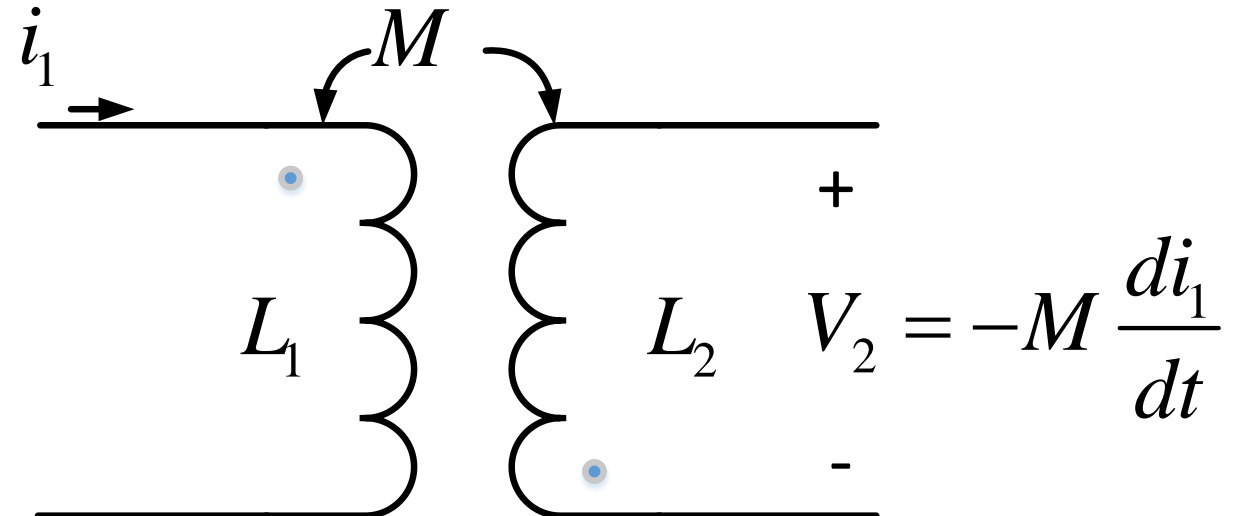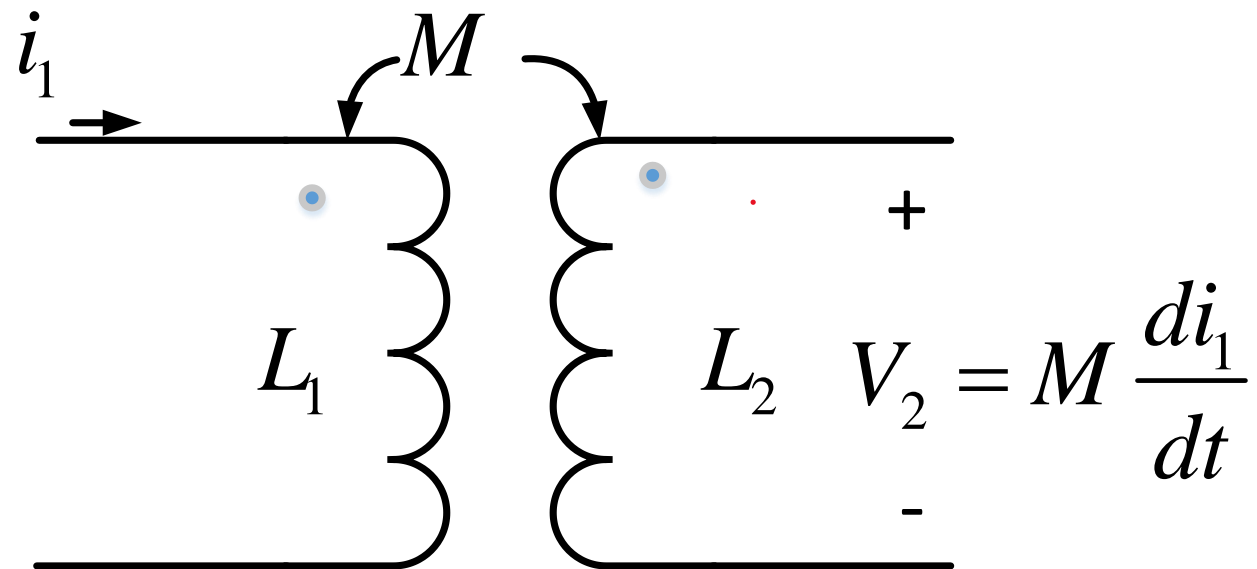




# Dot Convention (Contd..)

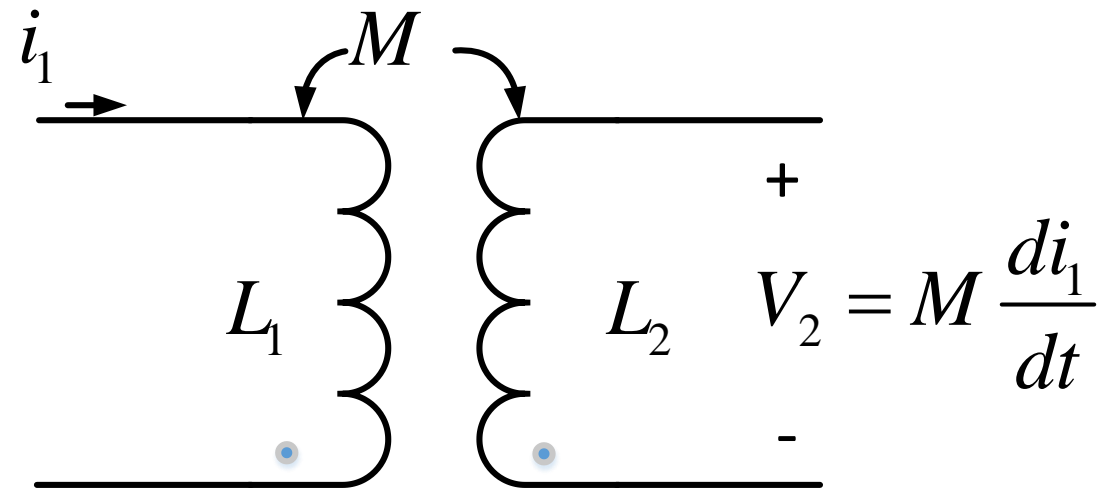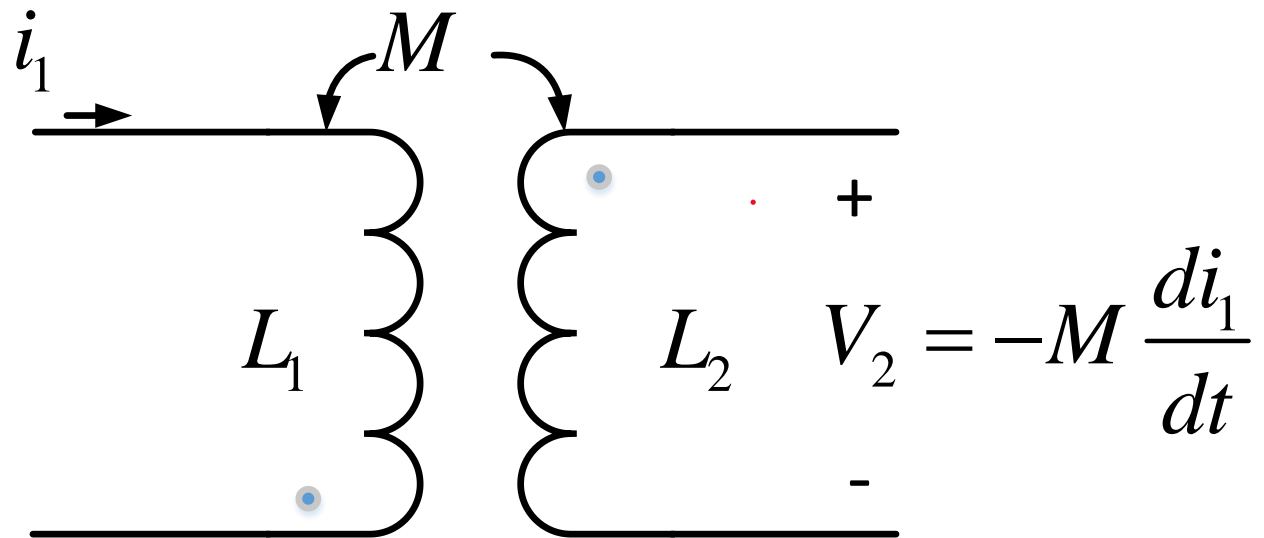

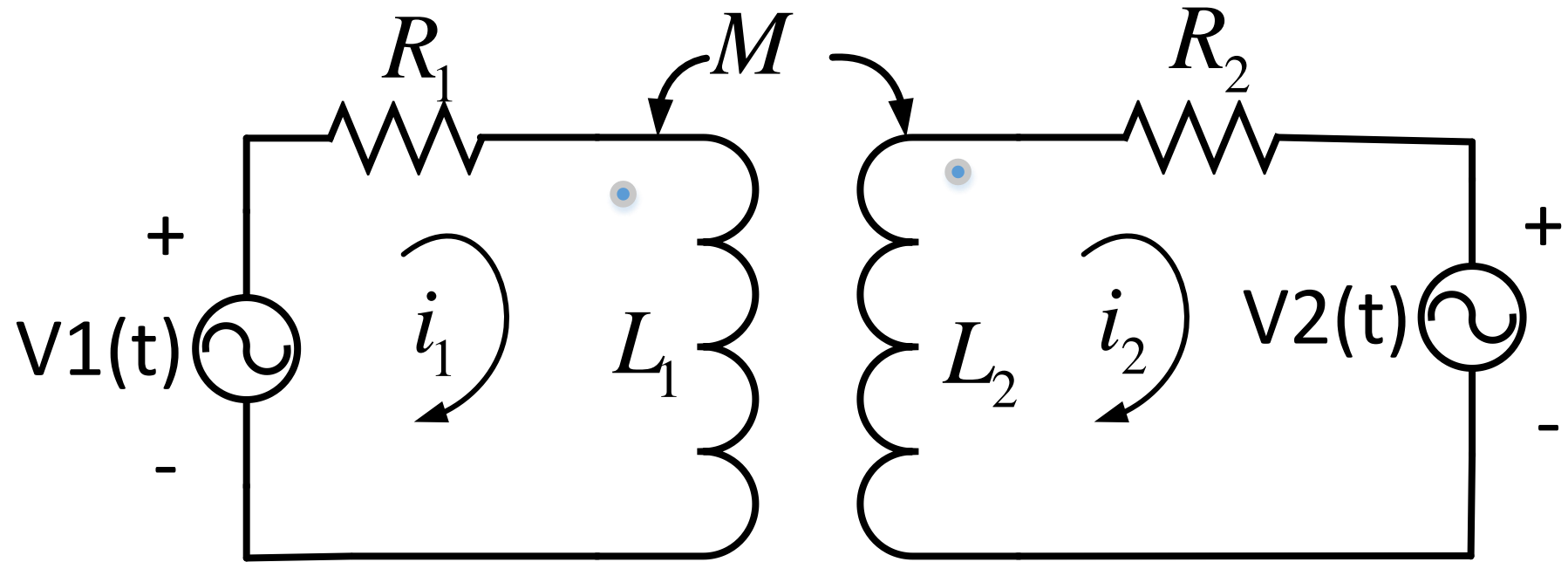
# Example 1

- Write the KVL equations for the coupling circuit.



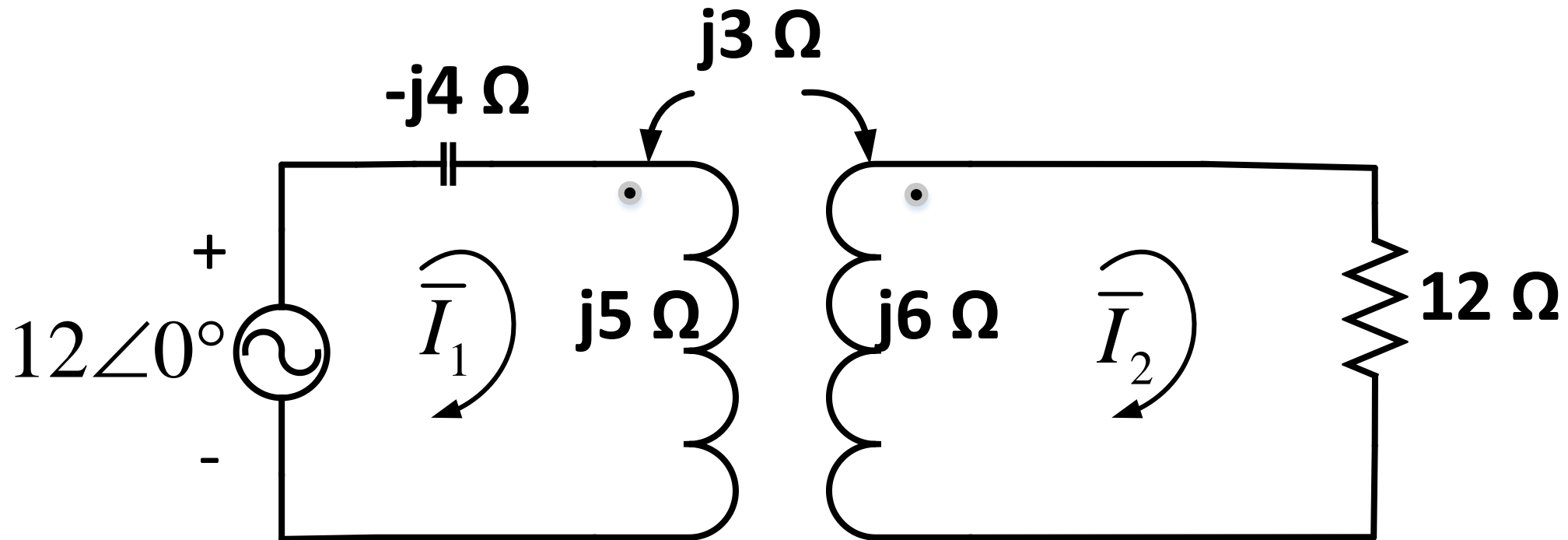
## Example 2

Calculate the phasor currents  $\bar{I}_1$  and  $\bar{I}_2$  in the following circuit.



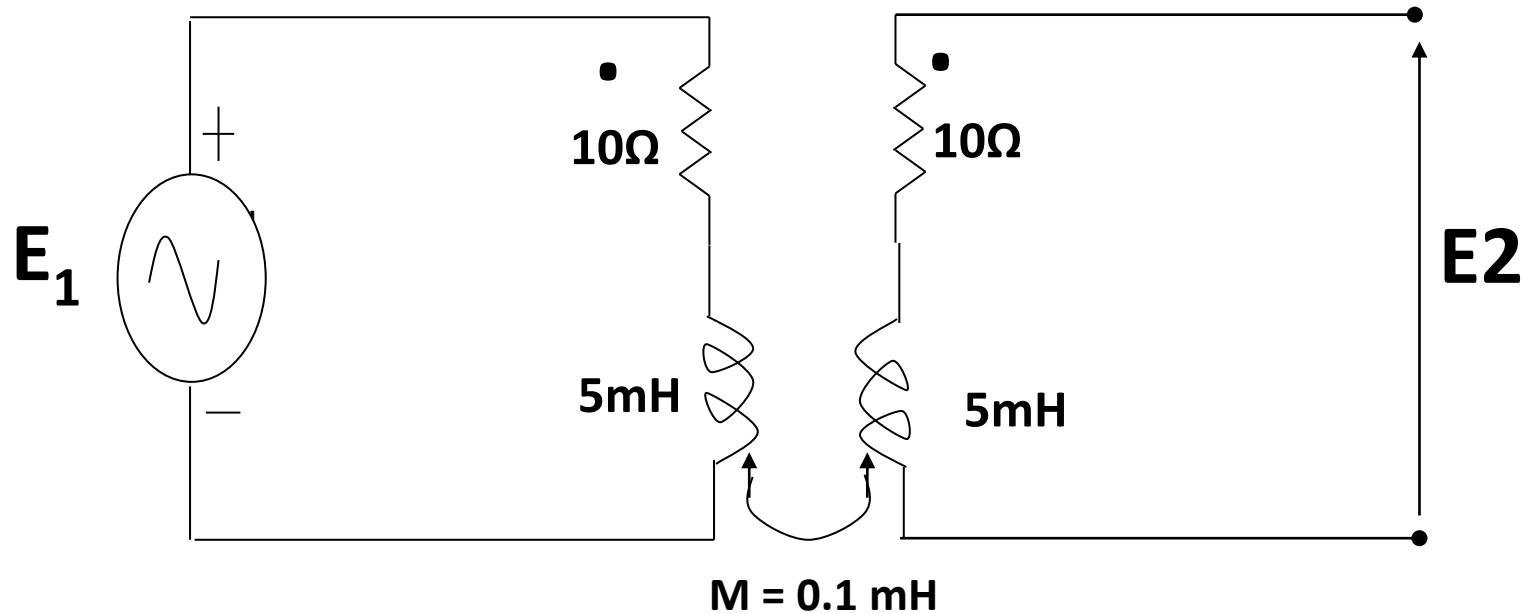
## Example 3

For the circuit shown below, determine the p.d.  $E_2$  which appears across the open-circuited secondary winding, given that  $E_1 = 8 \sin 1500t$  volts


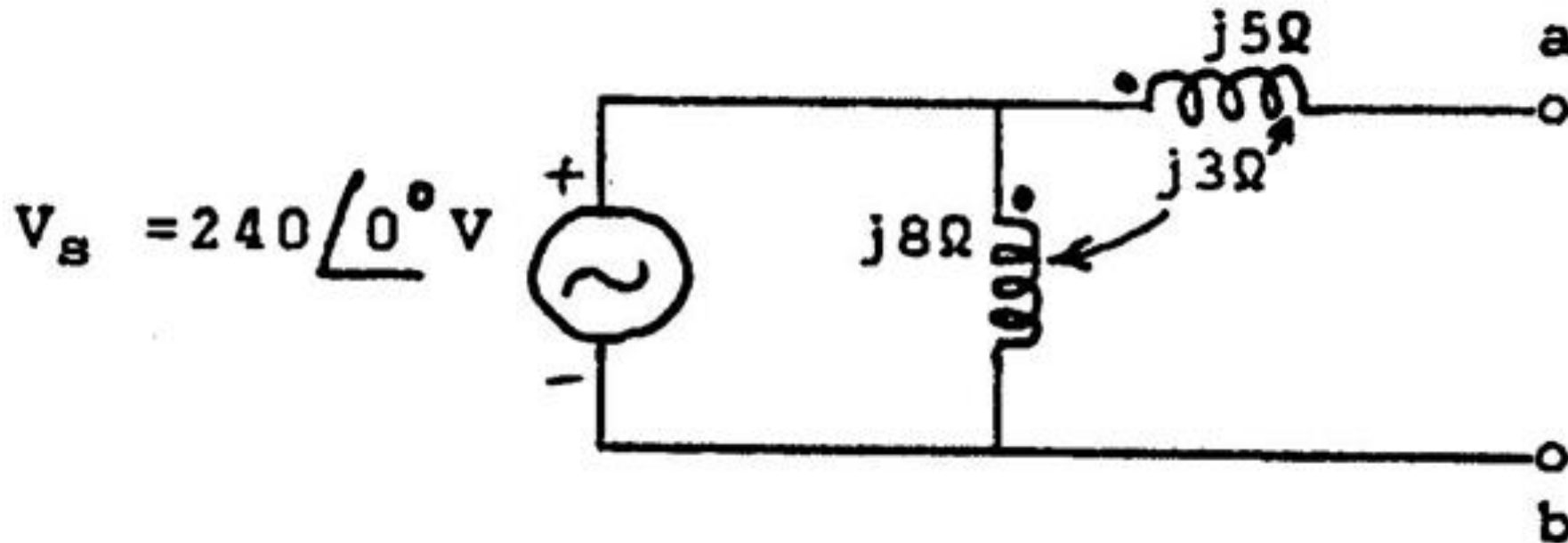
## Example 4

Find the Thevenin's equivalent between terminal a-b of the network shown in Fig. 1. Determine the current through a load of  $5-j20$  ohms connected between terminal a-b



# Coefficient of Coupling

- It is shown that the upper limit of mutual inductance is given by,

$$M \leq \sqrt{L_1 L_2}$$

- The extent to which M approaches its maximum forcible value is given by,

$$K = \frac{M}{\sqrt{L_1 L_2}}$$

- Where K is called the coefficient of coupling